


Bandpass filter transfer function

$$\begin{aligned} R &:= 10 & L &:= 0.001 & C &:= 1 \cdot 10^{-6} \\ \omega_0 &:= \frac{1}{\sqrt{L \cdot C}} = 3.162 \times 10^4 & \tau &:= R \cdot C = 1 \times 10^{-5} & Q &:= \omega_0 \cdot \tau = 0.316 \end{aligned}$$


$$h(\omega) := \frac{\frac{\omega}{\omega_0}}{\frac{\omega}{\omega_0} - i \cdot Q \cdot \left[1 - \left(\frac{\omega}{\omega_0} \right)^2 \right]}$$

Complex ratio of output voltage to input voltage

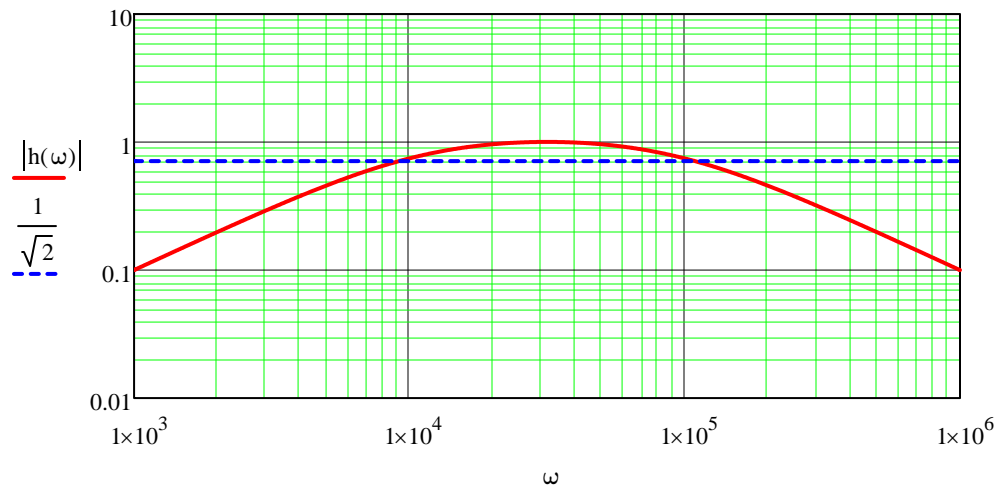Magnitude of Bandpass Filter Transfer Function



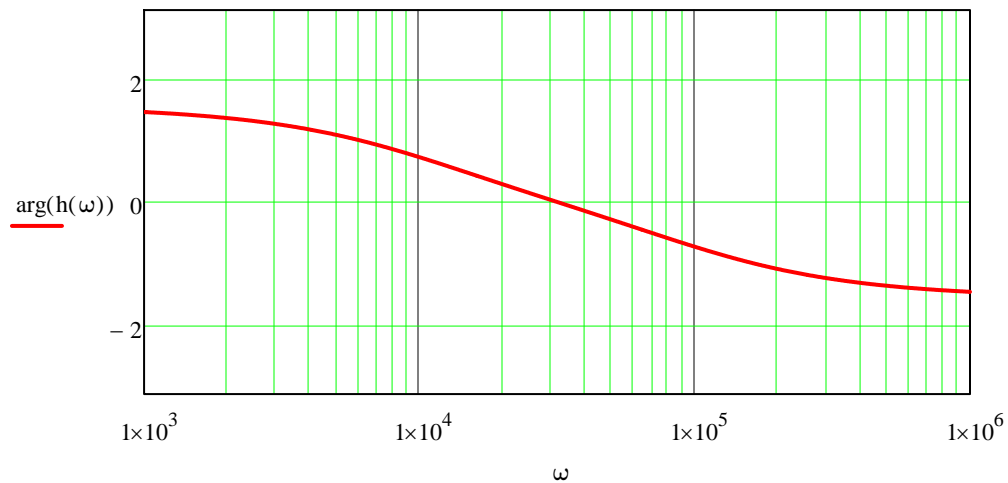Phase of Bandpass Filter Transfer Function



$$Q = 0.316$$

Prediction for the quality factor Q

$$f(x) := |h(x)| - \frac{1}{\sqrt{2}}$$

Numerical calculation of Q

$$\omega_1 := \text{root}(f(x), x, 0, \omega_0) = 9.161 \times 10^3$$

$$\omega_2 := \text{root}(f(x), x, \omega_0, 4\omega_0) = 1.092 \times 10^5$$

$$\frac{\omega_0}{\omega_2 - \omega_1} = 0.316$$

Definition of the Q factor