

Three Pole Butterworth Filter


$$L_1 := \frac{3}{2} \quad L_3 := \frac{1}{2} \quad R := 1 \quad C := \frac{4}{3}$$

$$Z(\omega) := \begin{bmatrix} i \cdot \left(\omega \cdot L_1 - \frac{1}{\omega \cdot C} \right) & \frac{-1}{i \cdot \omega \cdot C} \\ \frac{-1}{i \cdot \omega \cdot C} & R + i \cdot \left(\omega \cdot L_3 - \frac{1}{\omega \cdot C} \right) \end{bmatrix} \quad \underline{V} := \begin{pmatrix} 1 \\ 0 \end{pmatrix}$$

$$I(\omega) := Z(\omega)^{-1} \cdot \underline{V}$$

$$V_{\text{out}}(\omega) := I(\omega)_2 \cdot R$$

$$H(\omega) := |V_{\text{out}}(\omega)|$$

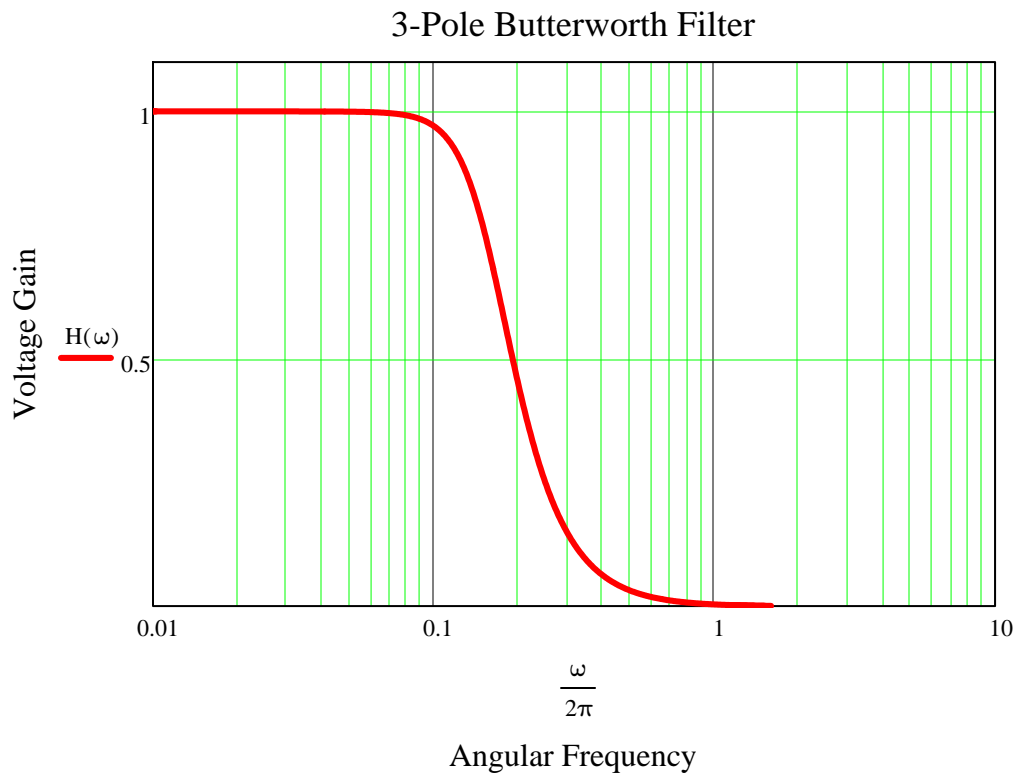

Plot the response in the complex frequency plane

$$F(x, y) := H(x + i \cdot y)$$

3-pole Butterworth filter response vs complex frequency

F

Note the locations of the 3 "poles", where there are zeroes in the complex impedance.