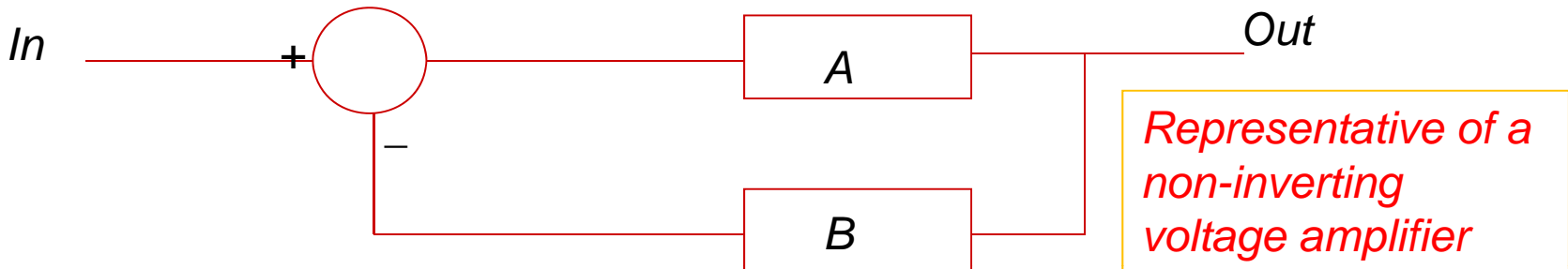


Physics 160

Lecture 15

R. Johnson
May 18, 2015

Negative Feedback Formalism



A = open loop gain (forward gain with no feedback), typically huge (e.g. 100,000)

B = gain of feedback network, typically < 1

AB = loop gain


$$V_{out} = A \cdot (V_{in} - B \cdot V_{out})$$

Feedback

$$G = \frac{V_{out}}{V_{in}} = \frac{A}{1 + AB} = \frac{1}{B} \left[\frac{1}{1 + (1/AB)} \right]$$

Ideally, you want the loop gain AB to be large, so that G is determined by only the feedback network gain B .

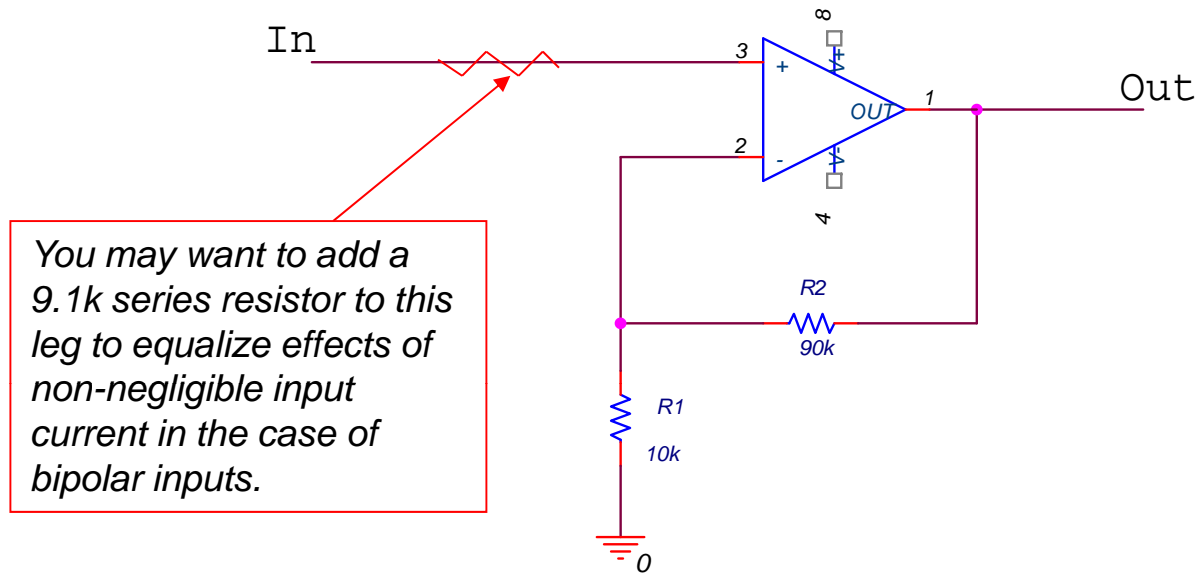Non-Inverting Amp, More Complete Analysis



Using the not-so-simplified analysis:


Suppose the forward gain is $A=10^5$ (fairly typical).

Here the feedback gain is $B=R_1/(R_1+R_2)=1/10$ (voltage divider).

Then the loop gain is $AB=10^4$.


$$G = \frac{V_{out}}{V_{in}} = 10 \times \left(\frac{1}{1 + 10^{-4}} \right) = 9.999$$

Example

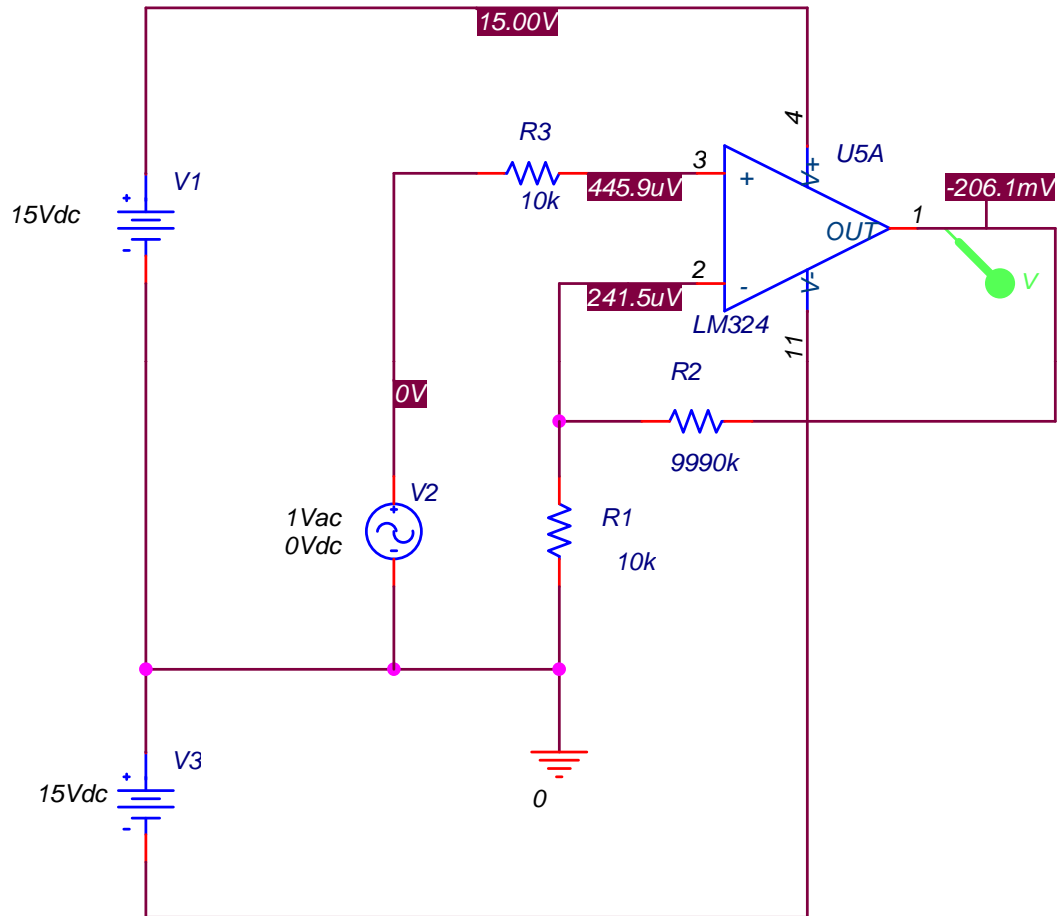

$$G = \frac{V_{out}}{V_{in}} = 1000 \times \left[\frac{1}{1 + (1000/A)} \right]$$

Non-Inverting Amp Output

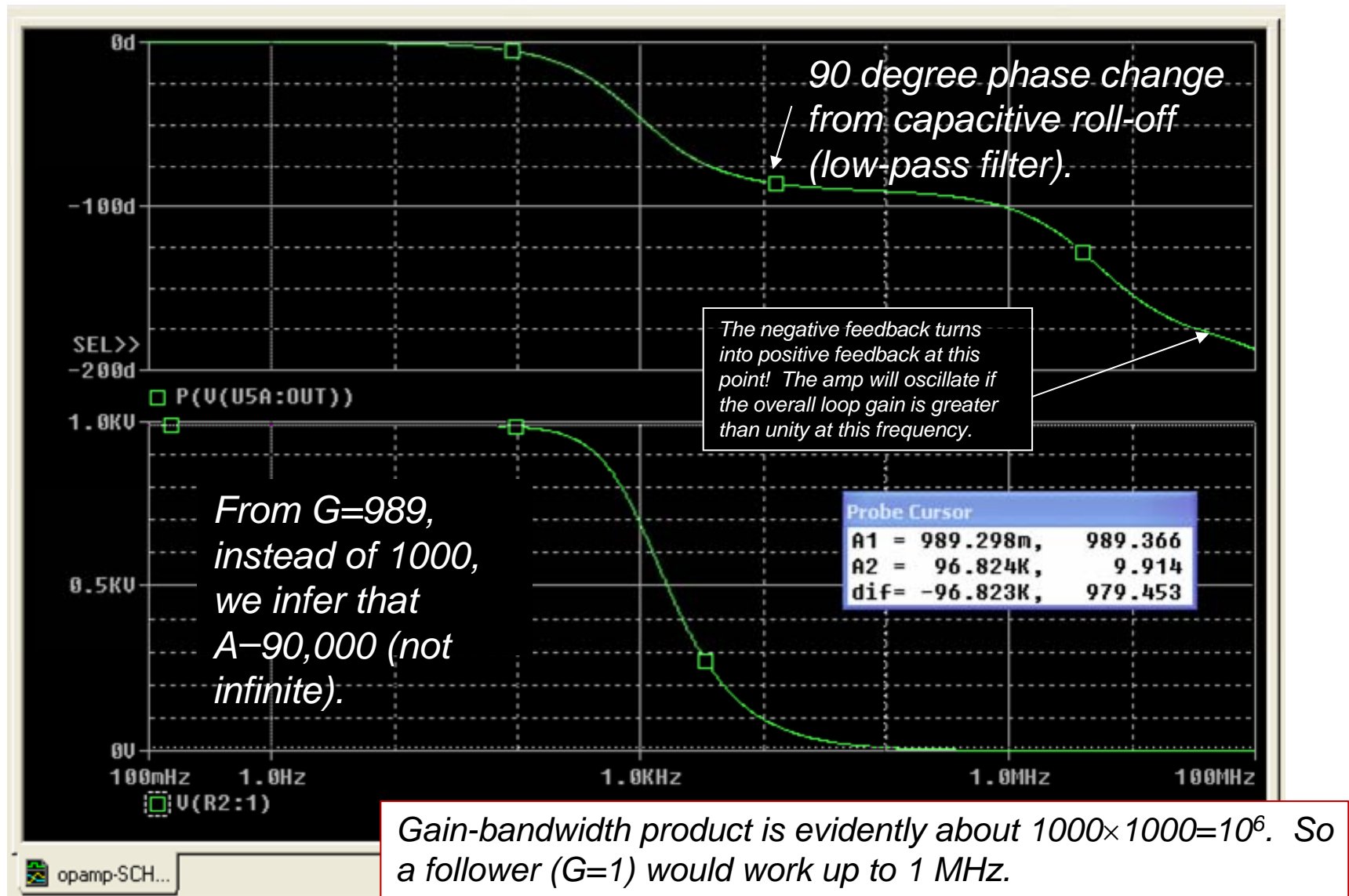

LM324 Data Sheet

http://www.onsemi.com/pub_link/Collateral/LM324-D.PDF


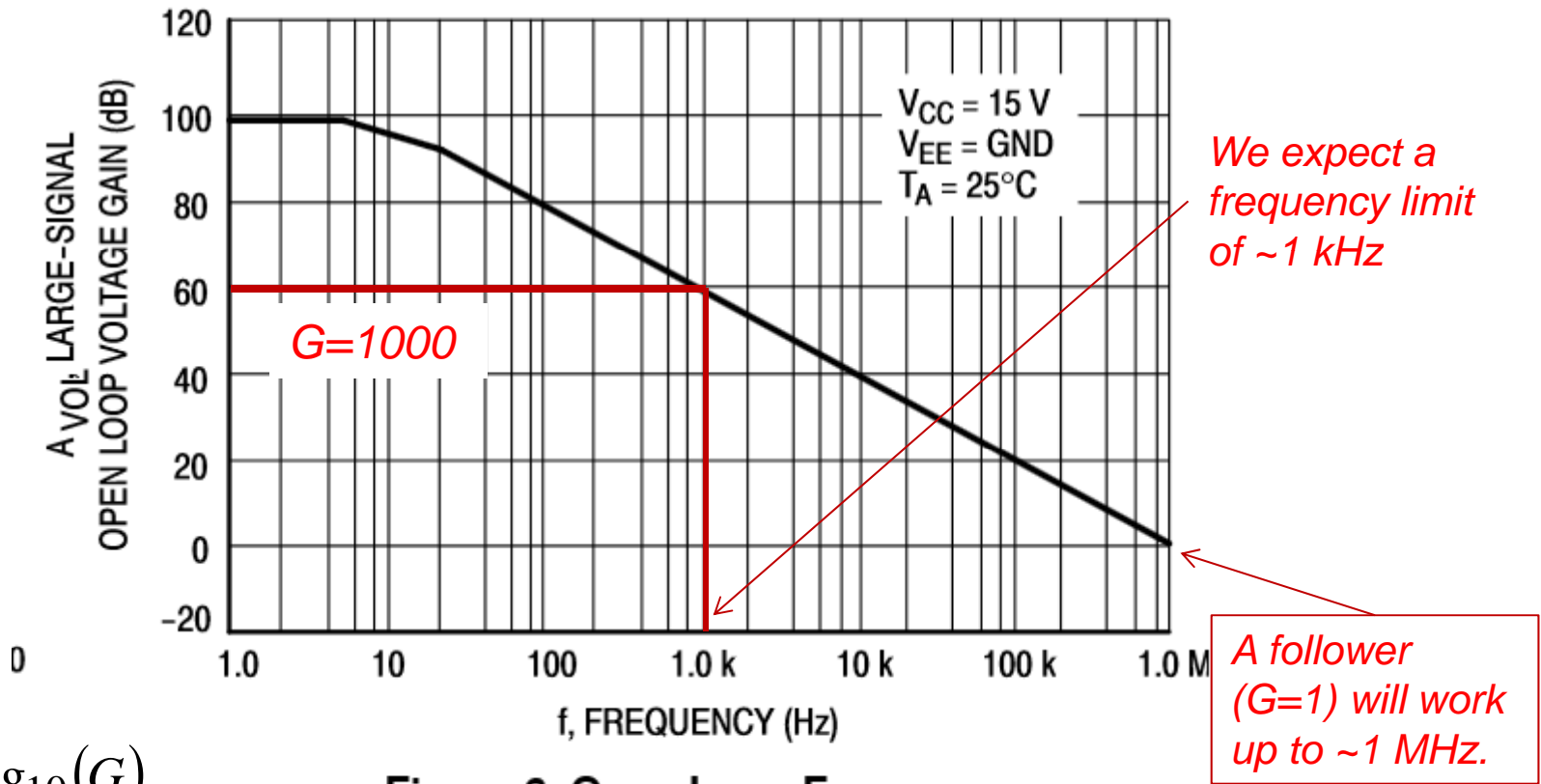


Figure 6. Open Loop Frequency

$$\text{dB} = 20 \cdot \log_{10}(G)$$

$$20 \cdot \log(90000) = 99 \text{ dB}$$

Follower

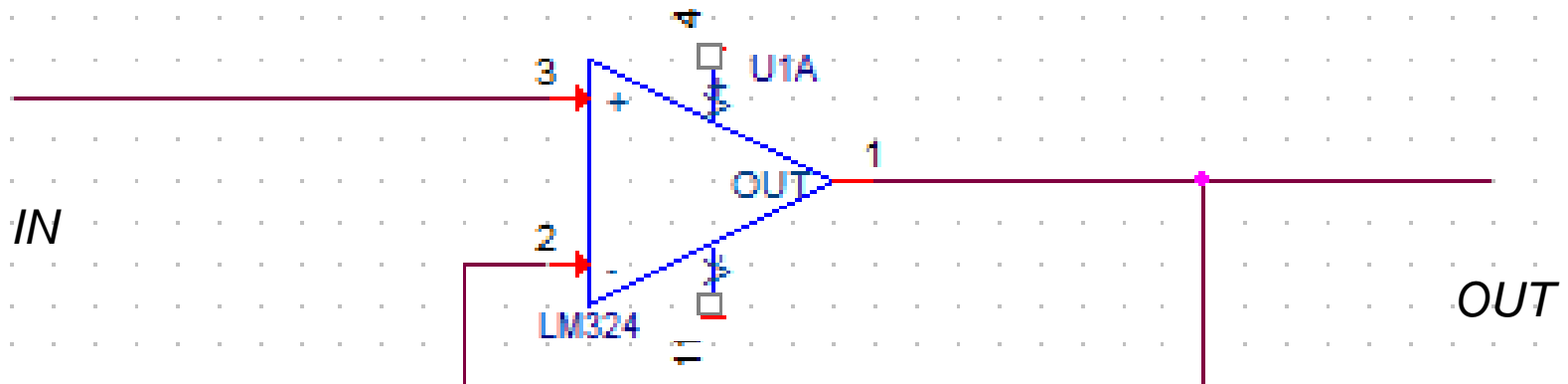


Non-inverting amp with 100% feedback. Be aware that the internal compensation capacitor is very important here to avoid high-frequency oscillations!

The LM324, like the LM411, has a large enough internal capacitor to enhance the Miller effect that it is stable when operated as a follower.

Some op amps require an external compensation capacitor, so you can optimize the operation.

AC Coupled Non-Inverting Amp

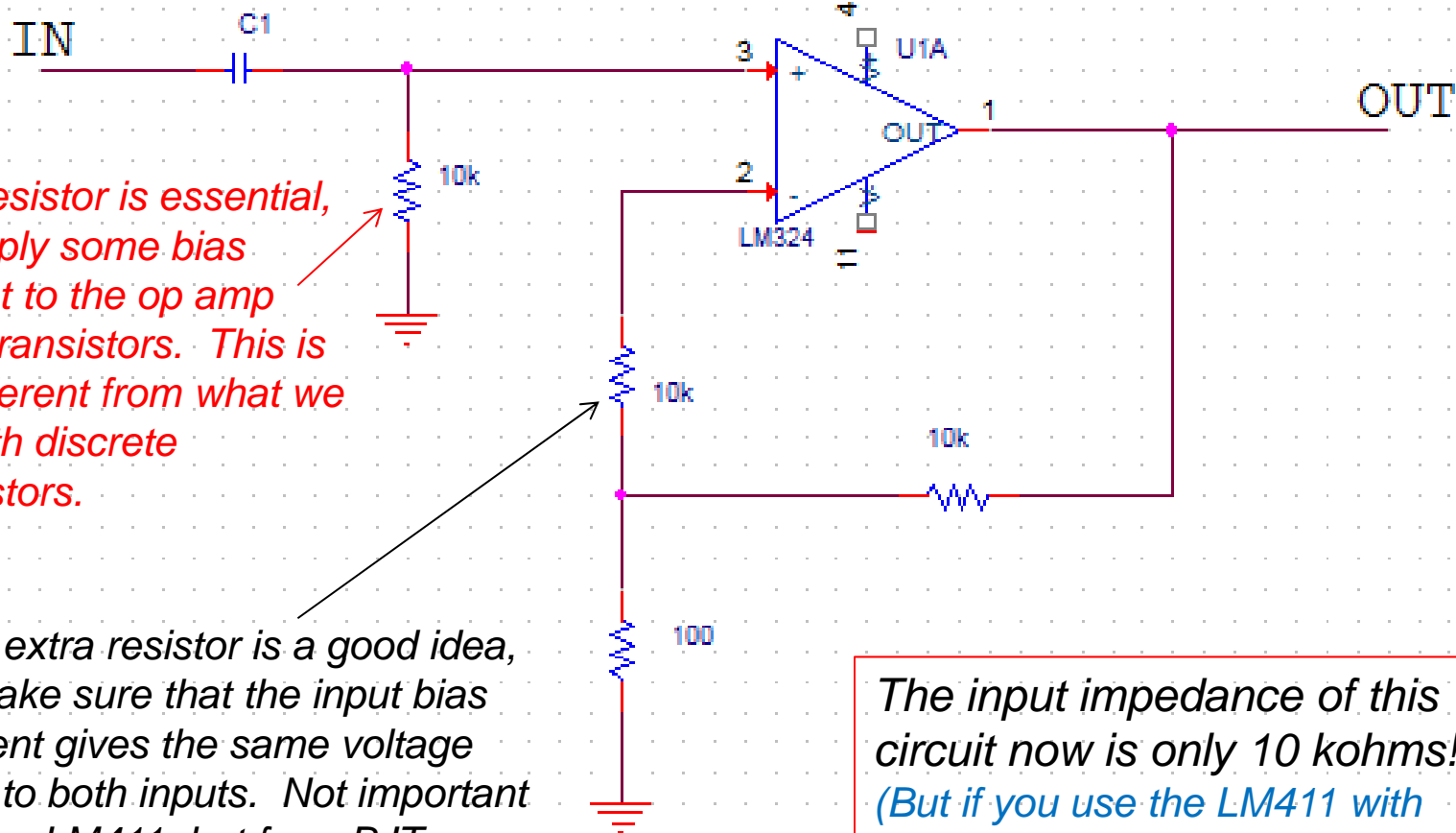(The op amp here is assumed to be operated with dual power supplies, so that the signal can oscillate about ground.)




This resistor is essential, to supply some bias current to the op amp input transistors. This is no different from what we did with discrete transistors.

This extra resistor is a good idea, to make sure that the input bias current gives the same voltage shift to both inputs. Not important for the LM411, but for a BJT op amp like the LM324 it can be very important.

The input impedance of this circuit now is only 10 kohms! (But if you use the LM411 with JFET inputs, the resistor can be much, much bigger.)


AC Coupled Follower with Bootstrap

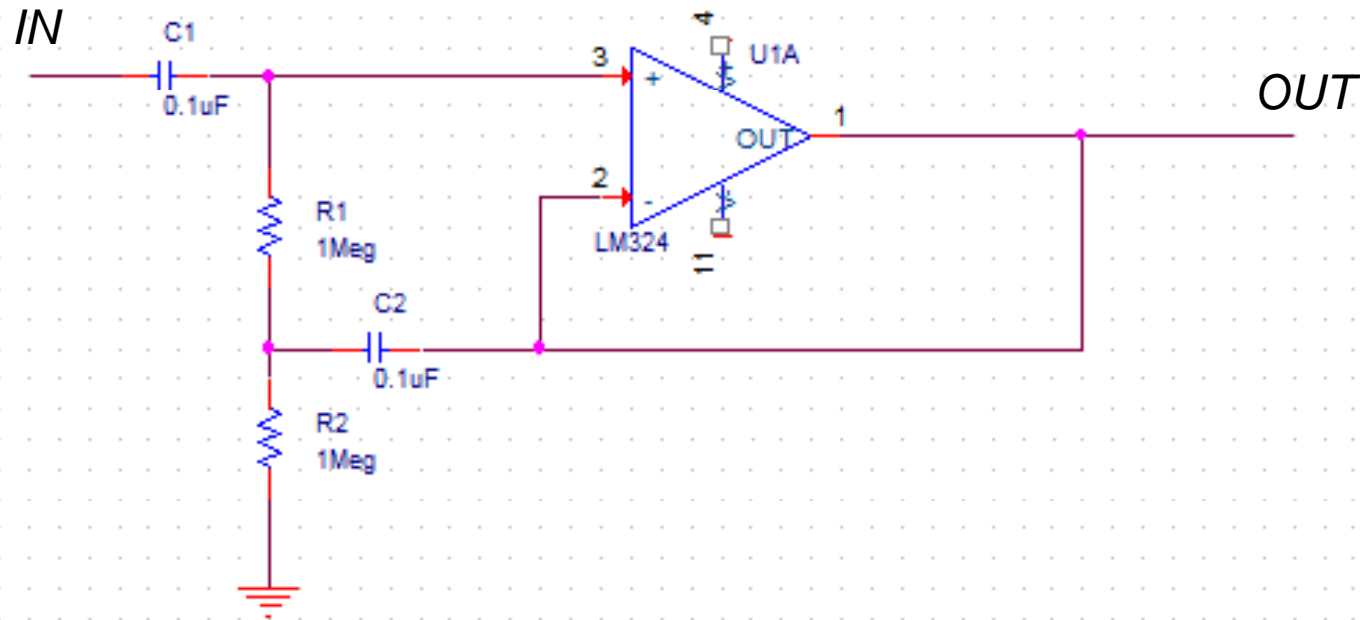

If necessary, for a follower the bias network can be bootstrapped as shown here, in exactly the same way as we did for the emitter-follower. (Note that this example is for an amplifier with both positive and negative supplies, so the inputs and outputs can be centered on ground potential.)

AC Non-Inverting Amplifier

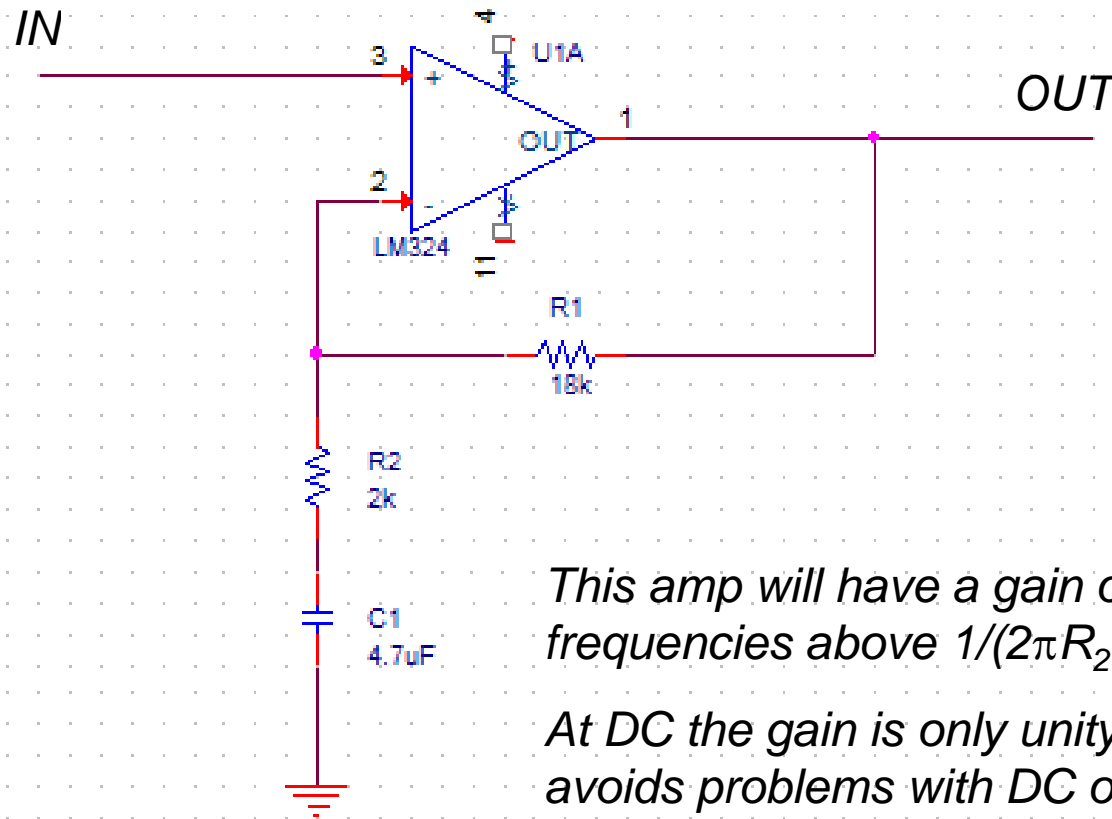
An alternative to using a coupling capacitor, or a good idea even if the input is AC coupled.



This amp will have a gain of 10 at frequencies above $1/(2\pi R_2 C_1)$.

At DC the gain is only unity, which avoids problems with DC offsets getting amplified.

Inverting Amp, More Complete Analysis

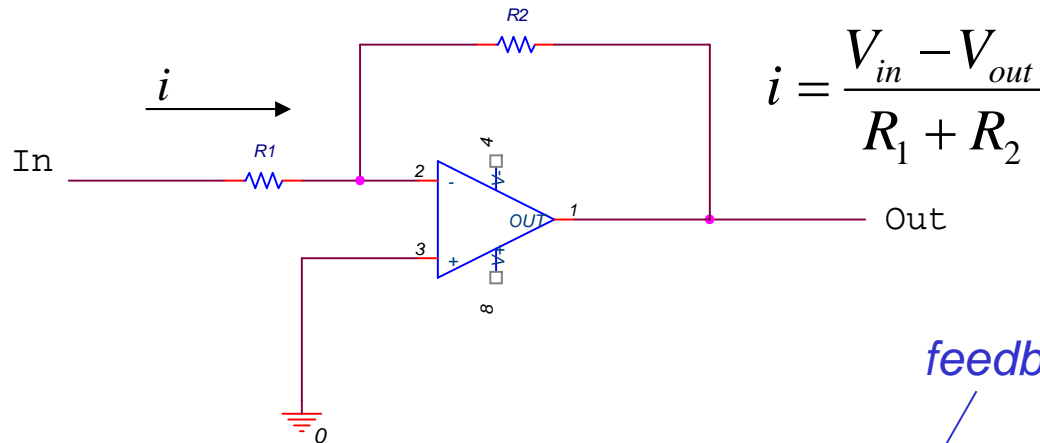

$$i = \frac{V_{in} - V_{out}}{R_1 + R_2}$$

Without R_1 this is a transresistance amplifier.


feedback

$$V_- = V_{in} - iR_1 = V_{in} - (V_{in} - V_{out}) \cdot B \quad \text{where} \quad B \equiv \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A \cdot (V_+ - V_-) = -AV_- \quad \text{Forward gain}$$


$$\text{Eliminate } V_- : \quad G = \frac{V_{out}}{V_{in}} = - \left[\frac{(1/B) - 1}{1 + 1/AB} \right] \approx - \frac{R_2}{R_1}$$

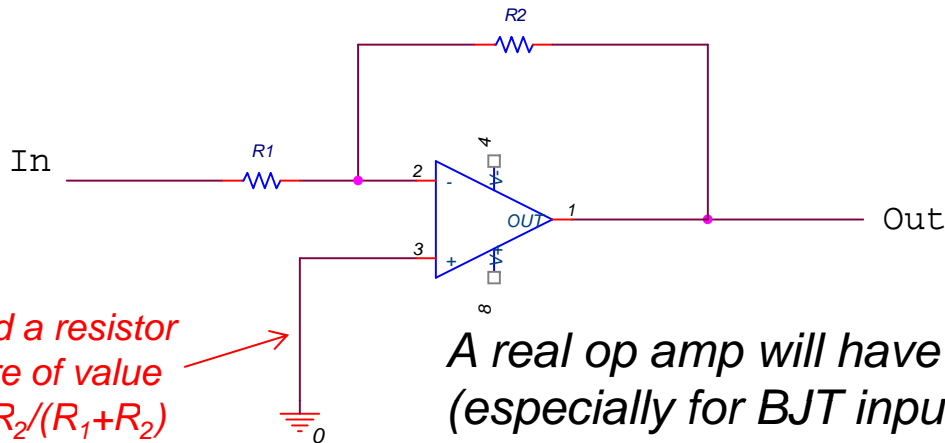Inverting Amp, Input Current Compensation




Add a resistor here of value $R_1 R_2 / (R_1 + R_2)$

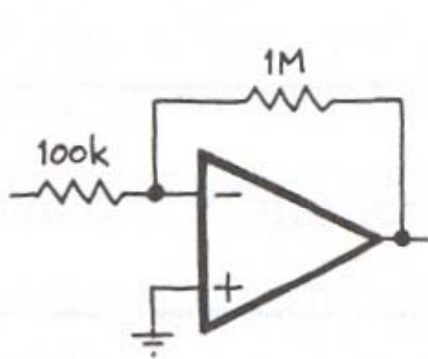
A real op amp will have some input bias current (especially for BJT input). The current flowing through R_1 and R_2 will shift the voltage at the inverting input. We should add a resistor to the non-inverting input to compensate:



bad

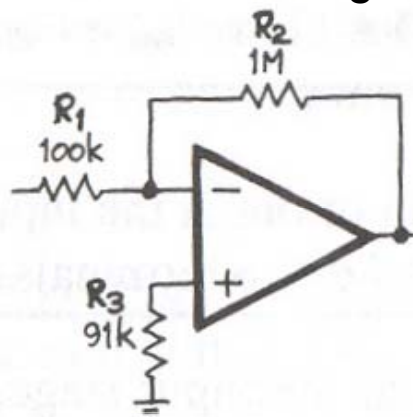

balanced

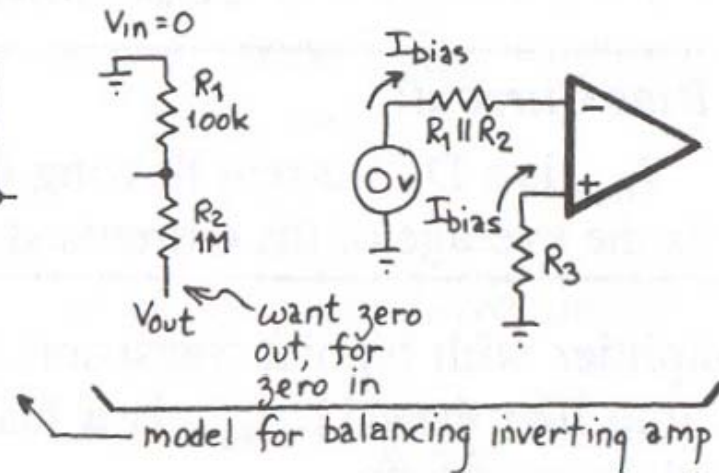

Analog Computing

Analog computing:

- *Integrator*
- *Differentiator*
- *Summing amplifier*
- *Log amp*


Op-amps provide nearly ideal performance for these devices, far, far beyond what can be achieved with passive components.

(Note: historically analog computers were widely used, but by now digital computers have such high performance and low cost that analog computers are largely obsolete.)



A 1960 Newmark analog computer, made up of five units. This computer was used to solve differential equations and is currently housed at the Cambridge Museum of Technology (from Wikipedia).


Integration Example

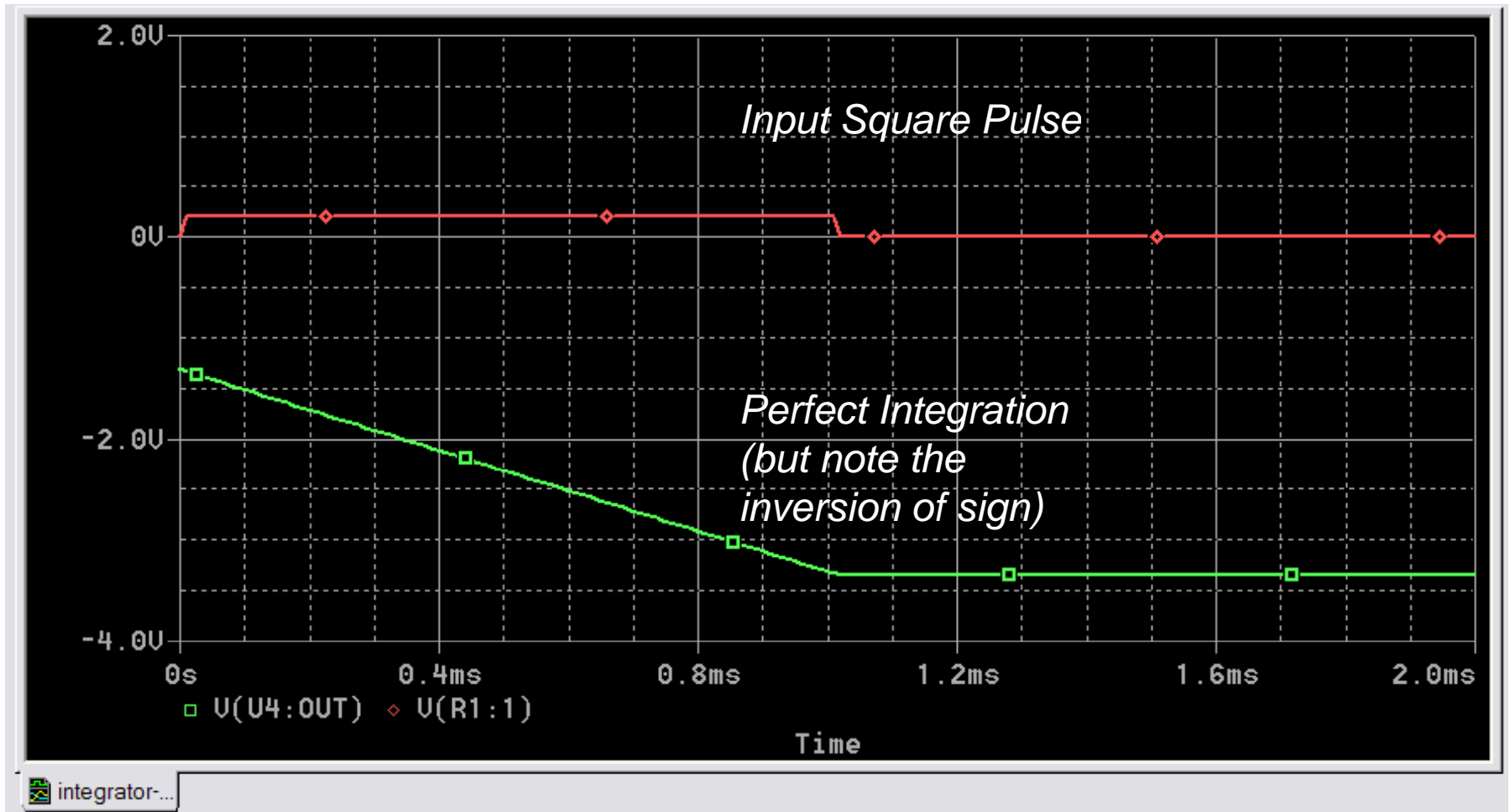


Differentiator

$$i_{in} = \frac{dQ}{dt} = C_2 \frac{dV_{in}}{dt}$$
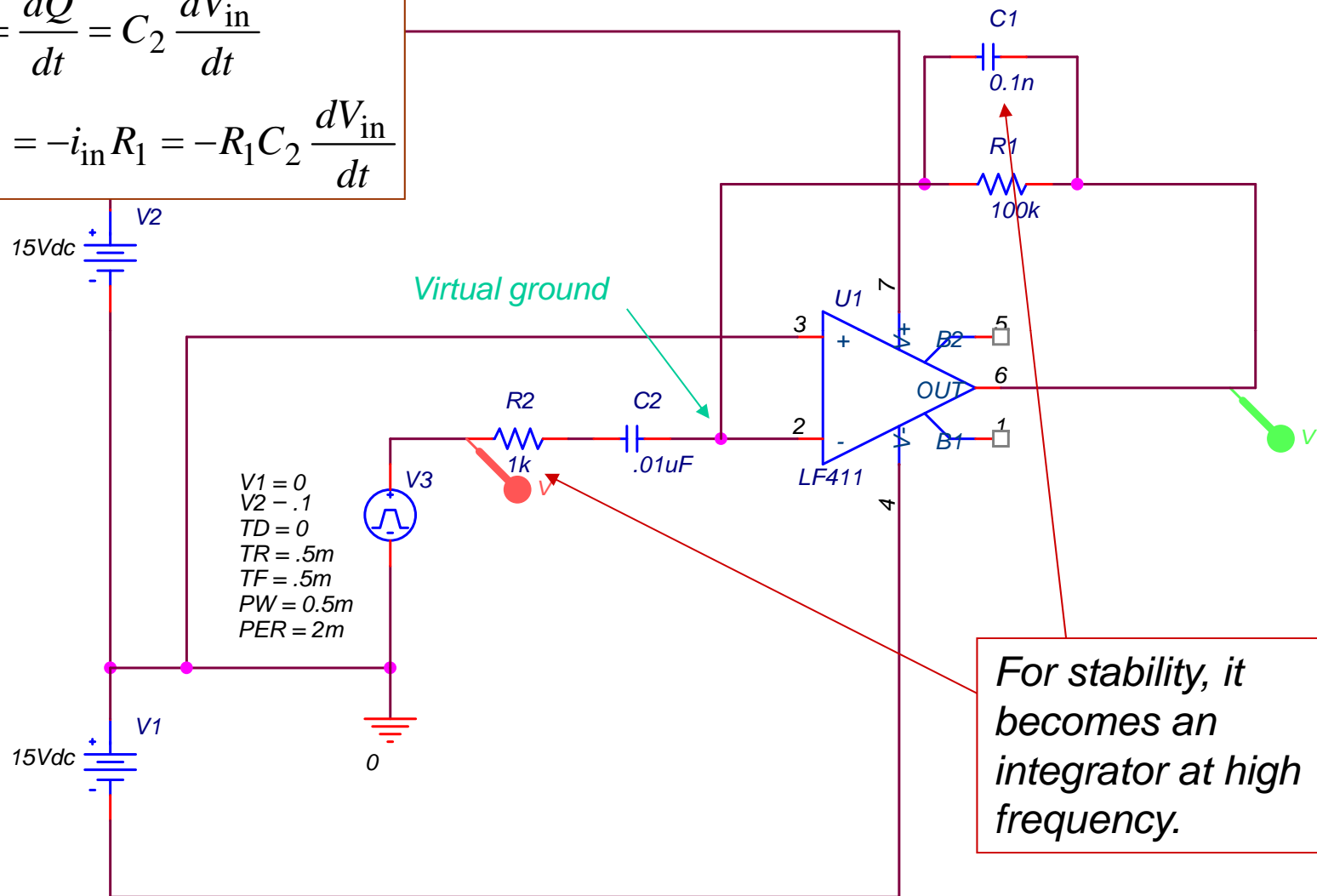
$$V_{out} = -i_{in} R_1 = -R_1 C_2 \frac{dV_{in}}{dt}$$



Differentiation Example

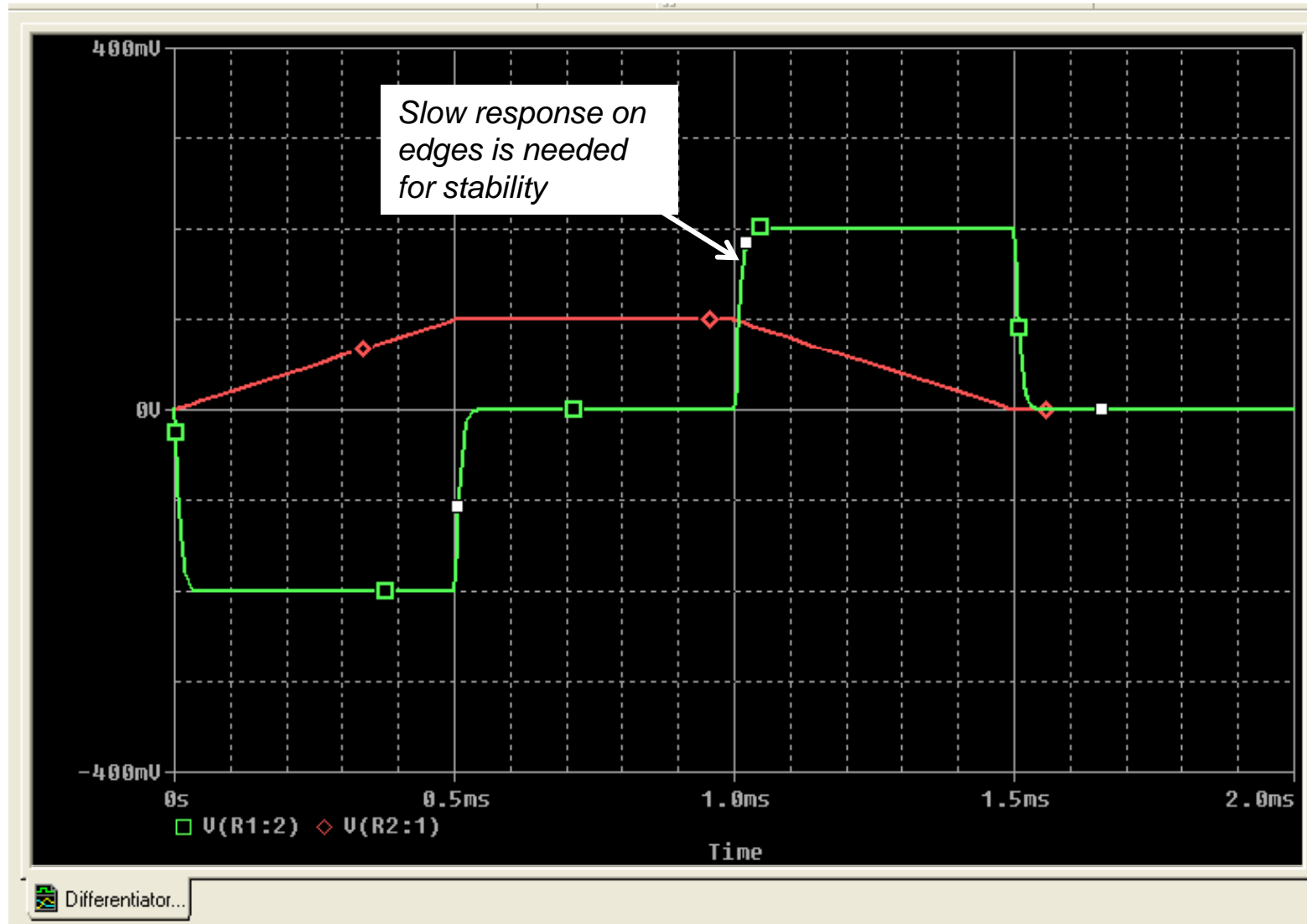


Stability Issues

- **Integrator:**
 - voltage gain *falls* at 6 dB per octave as frequency increases.
 - inherently **stable** against oscillations even with an uncompensated op-amp.
 - the feedback itself looks like Miller-effect frequency compensation.
- **Differentiator:**
 - voltage gain *rises* at 6 dB per octave as frequency increases.
 - inherently **unstable** against oscillations.
 - the gain must be rolled off at high frequency by introducing an integration, or oscillation is guaranteed!

$$\text{Integrator: } G = -\frac{1}{j\omega RC}$$

$$\text{Differentiator: } G = -j\omega RC$$

Sum (or Subtraction) Amp

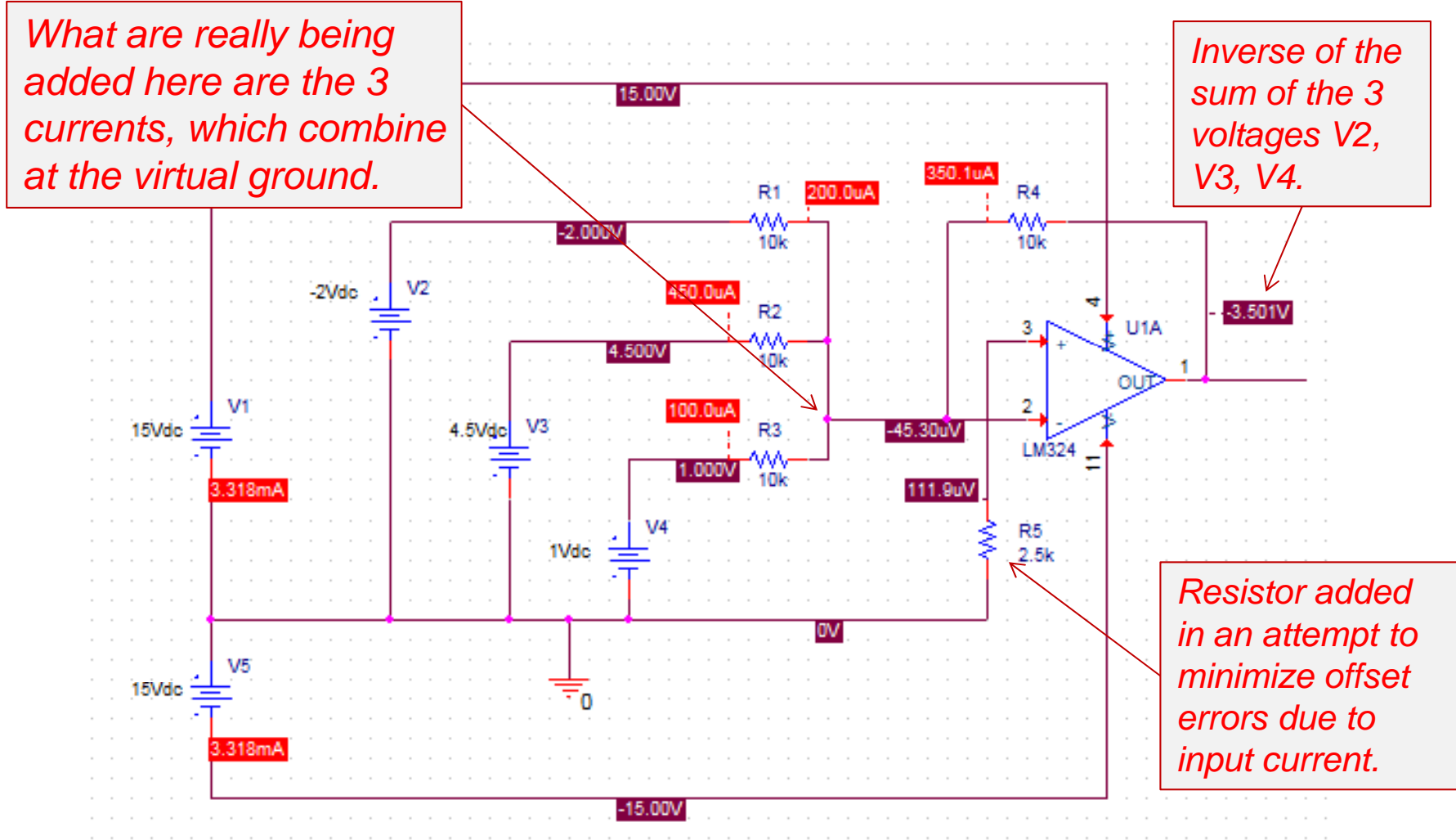

Log Amp

Diode is to protect against base-emitter breakdown in case input goes negative.

Emitter voltage is logarithm of collector current.

FET inputs for nearly zero current error.

Source of ~constant current.

Do DC scan of this source. Output will be the log of this input.

Constant current. Diode drop here provides temperature compensation.

× 16 non-inverting amp

With a log amp you can do analog multiplication and division!


Ebers-Moll: $V_{BE} = V_T \cdot \log(I_C + I_S) - V_T \cdot \log I_S$ But $I_C \gg I_S$

$$I_C = V_{in} / R_1$$


$$V_{out} = C + V_{BE} \cdot 16 \approx C - 0.96 \text{ V} \times \log_{10}(I_C / I_S)$$

Log Amp DC Bias Example

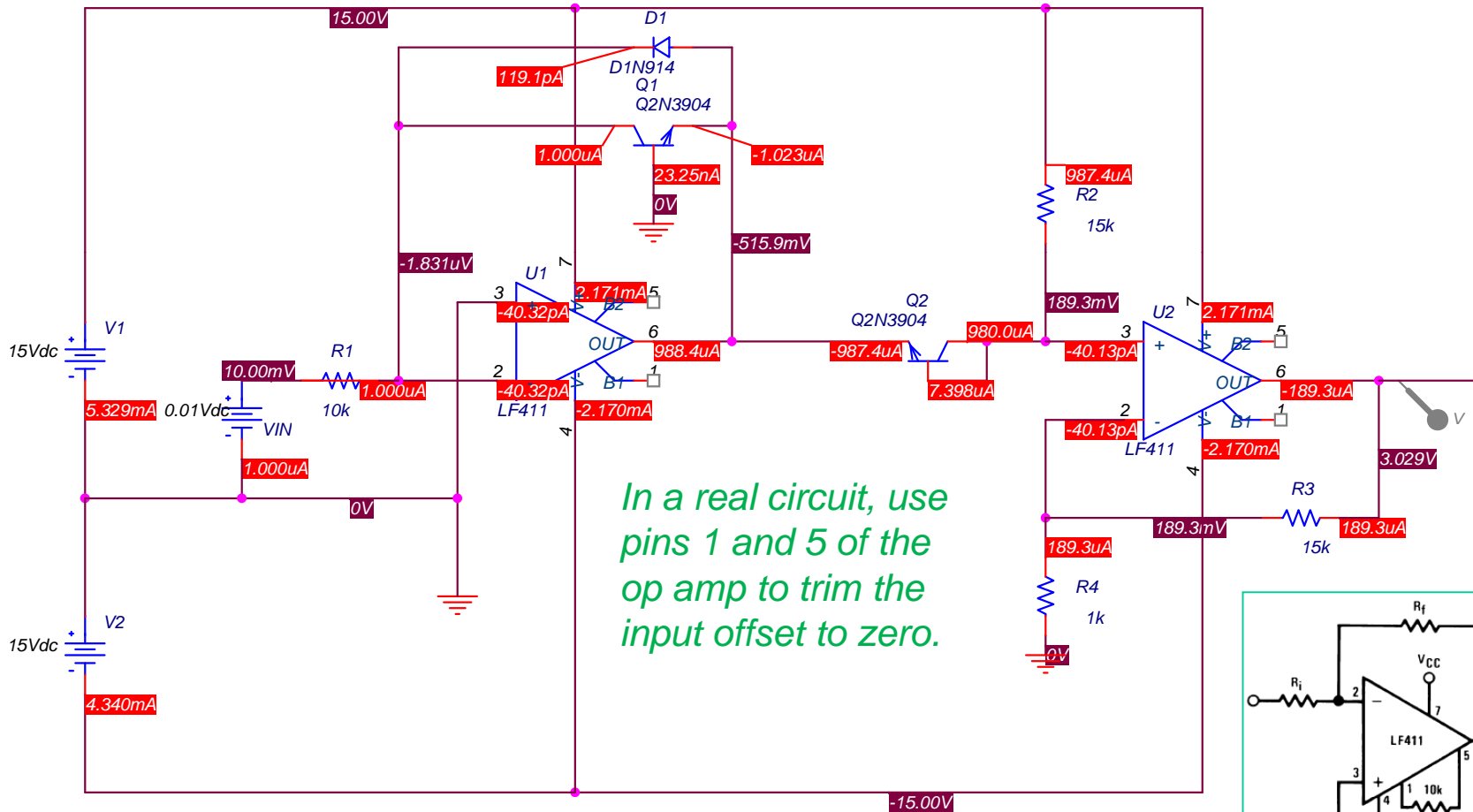
In a real circuit, put a capacitor in parallel with the diode, for stability.



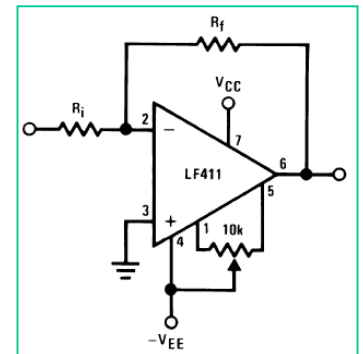In a real circuit, use pins 1 and 5 of the op amp to trim the input offset to zero.



Log Amp Simulation

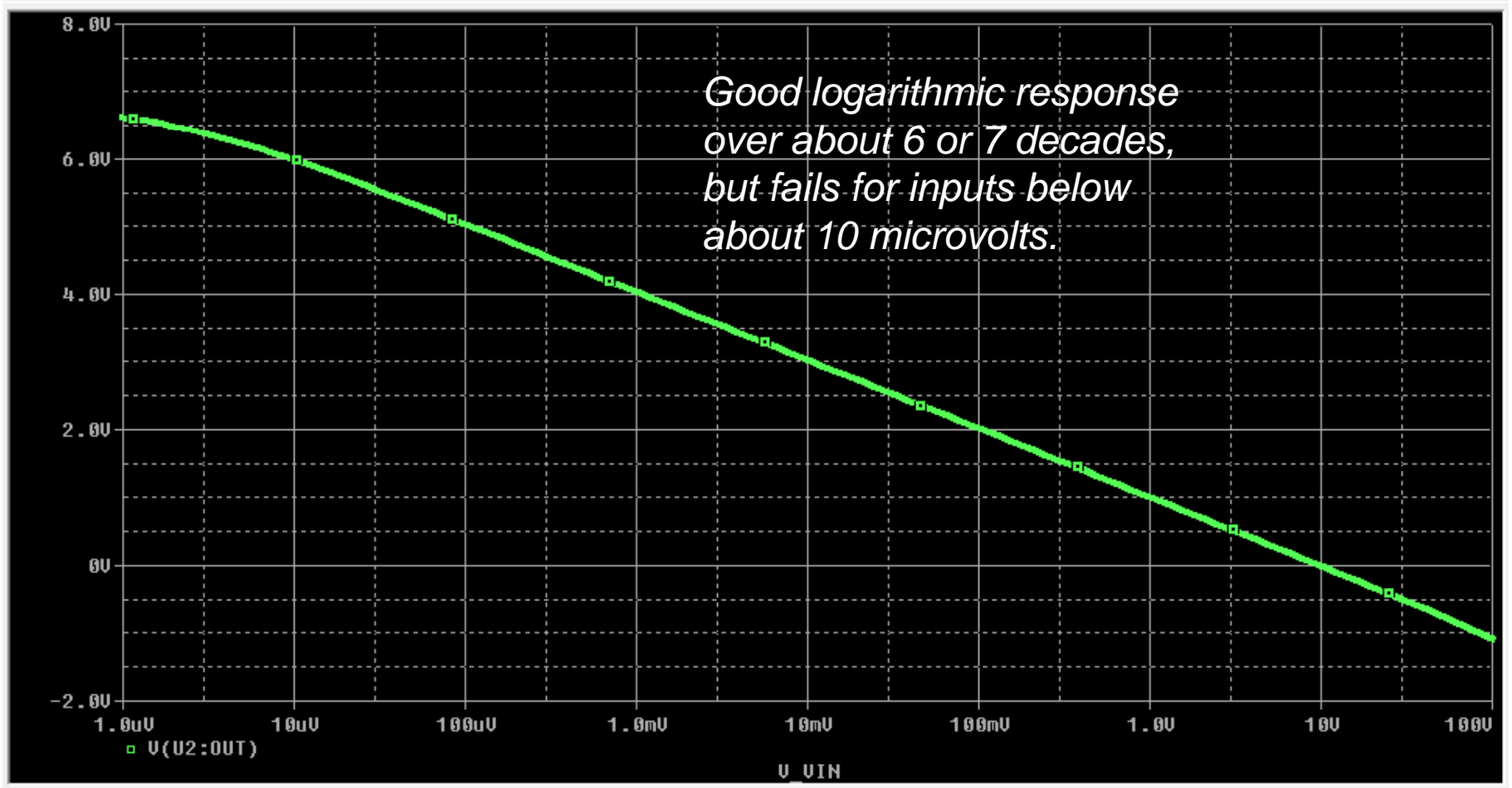


Behavior, Limitations of Real Op-amps

- *Input offset voltage*
- *Input current, and input-current mismatch*
 - *Design to minimize voltage offsets from this current*
 - *Input offset current*
- *Temperature dependences*
- *Slew rate*
 - *e.g. correcting crossover distortion*
- *Frequency range (gen. purpose op amps are not for high frequencies)*
- *Voltage gain and phase shift*
 - *Stability!*
- *CMRR and Common-mode input range*
- *Input impedance with negative feedback is extremely high*
- *Output impedance with negative feedback is very low*
 - *What is really relevant is the limitation on output current drive*
- *Output range (how close can the output get to the supply rails?)*
 - *Single-supply op amps; can the output slew all the way to zero?*

See the data sheet for the LF411 (posted on the course web page).

Offset Voltage and Input Current

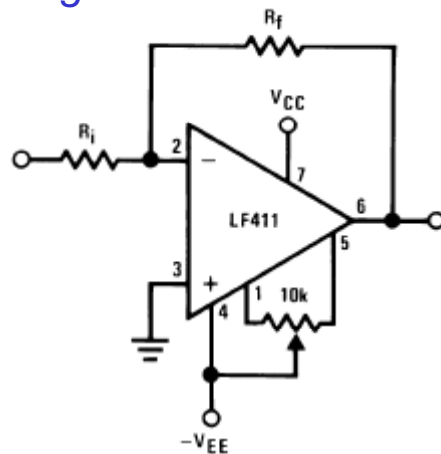
- *Offset voltage*
 - *2 mV max. for the 411*
 - *This is the effective mismatch at the input. At the output it gets multiplied by the gain!*
 - *Trimming*



- *Temperature and time drifts*


- *Input currents (esp. for BJTs)*
 - *Balancing resistors on inputs*
 - *Input offset current*

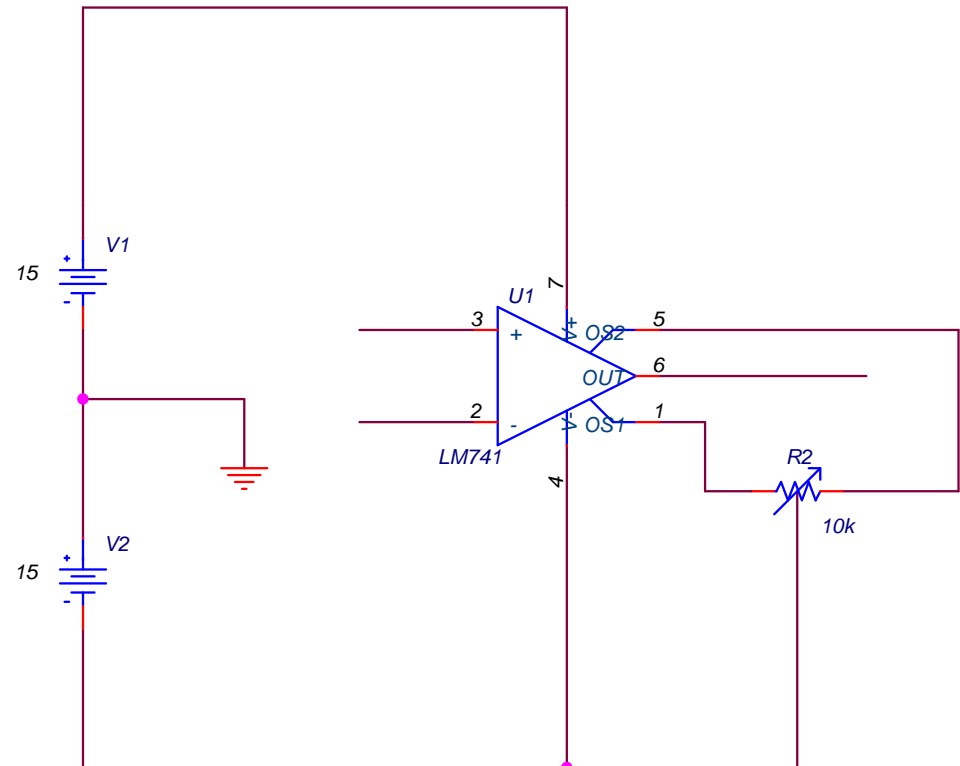- *A/C Amp: reduce DC gain to unity to minimize offset effects*




Charge Sensitive Amp

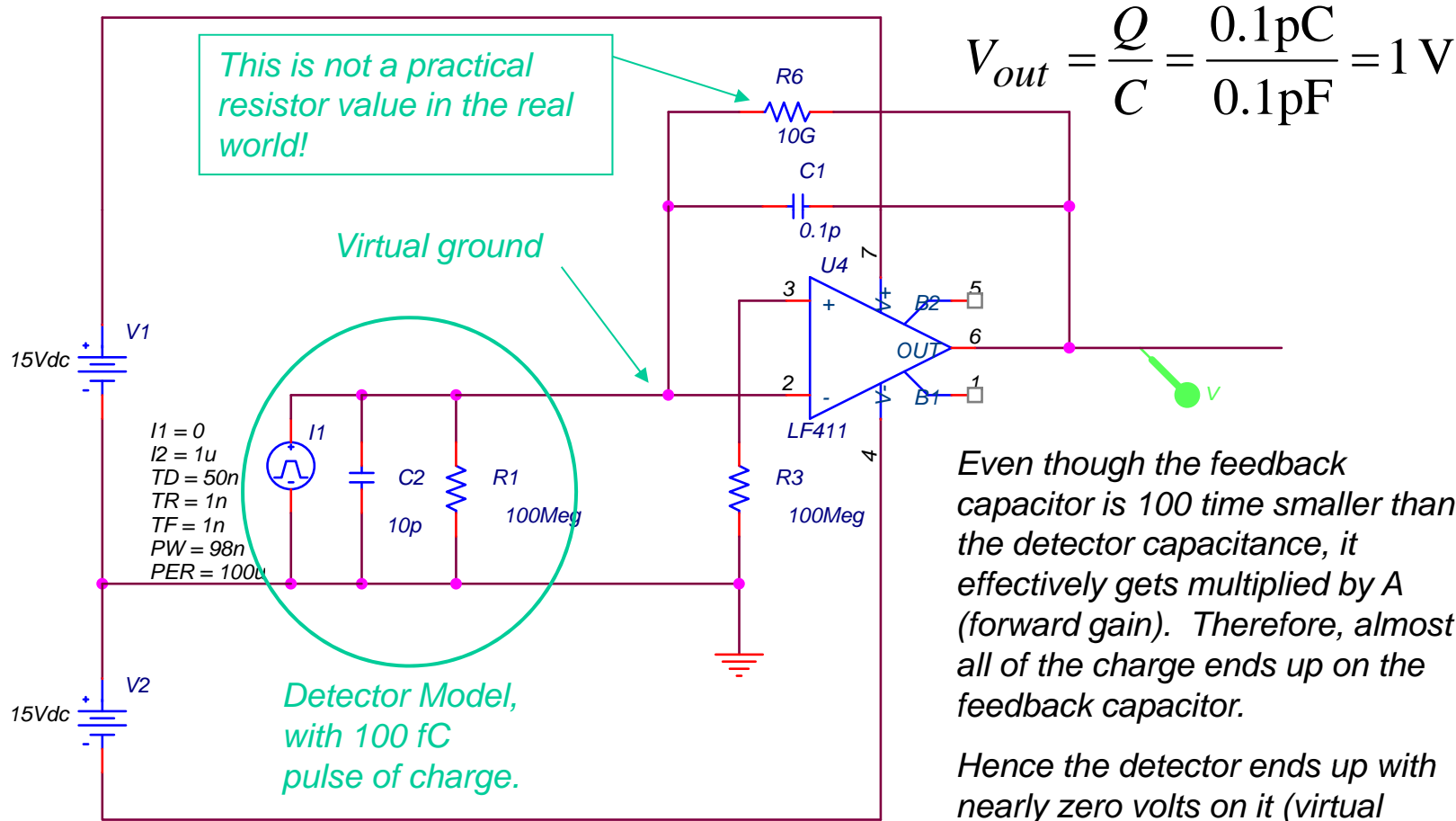- Integrate the pulse of current from a detector to produce an output voltage proportional to the total charge.




Charge Amp Example

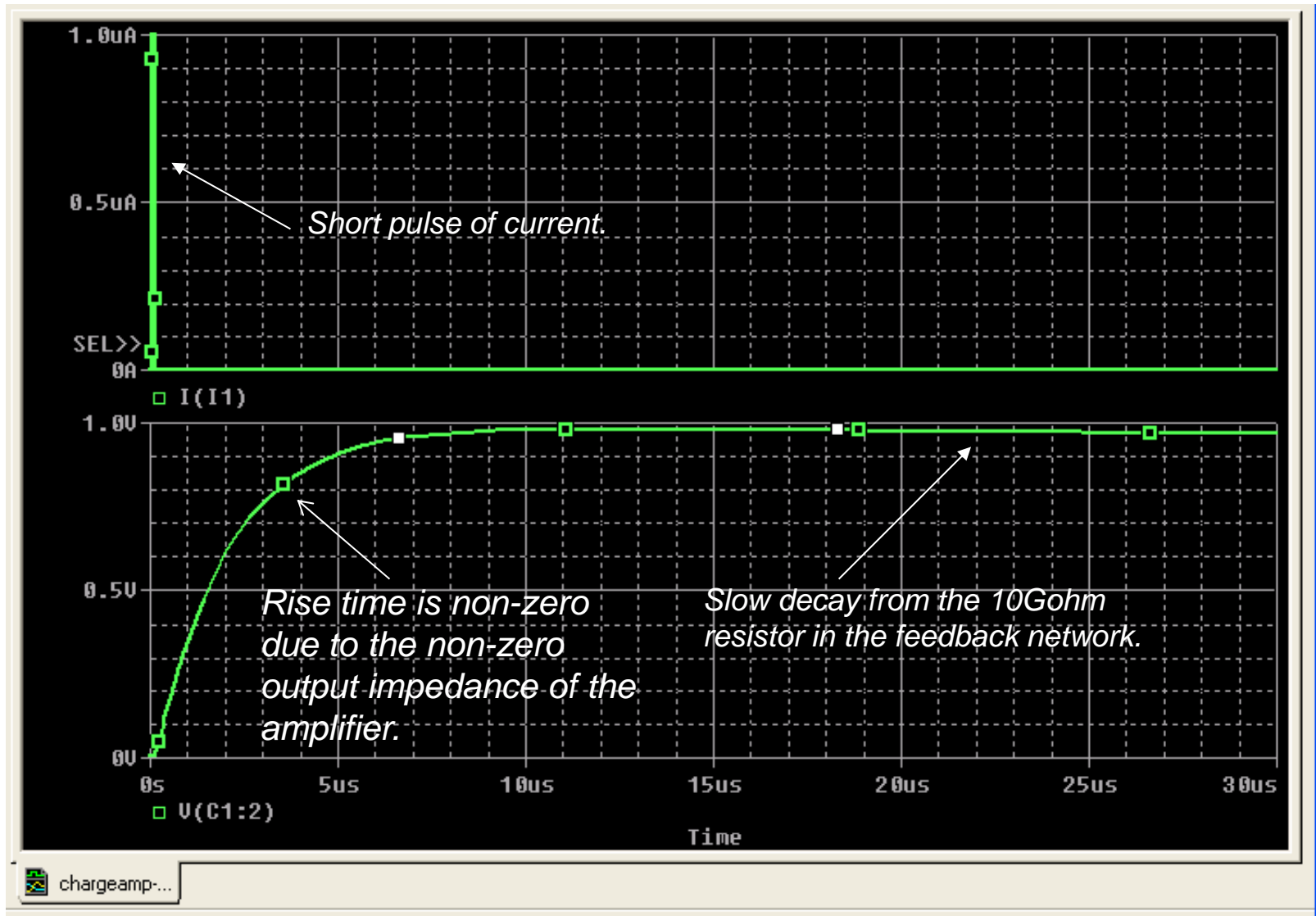

T Network

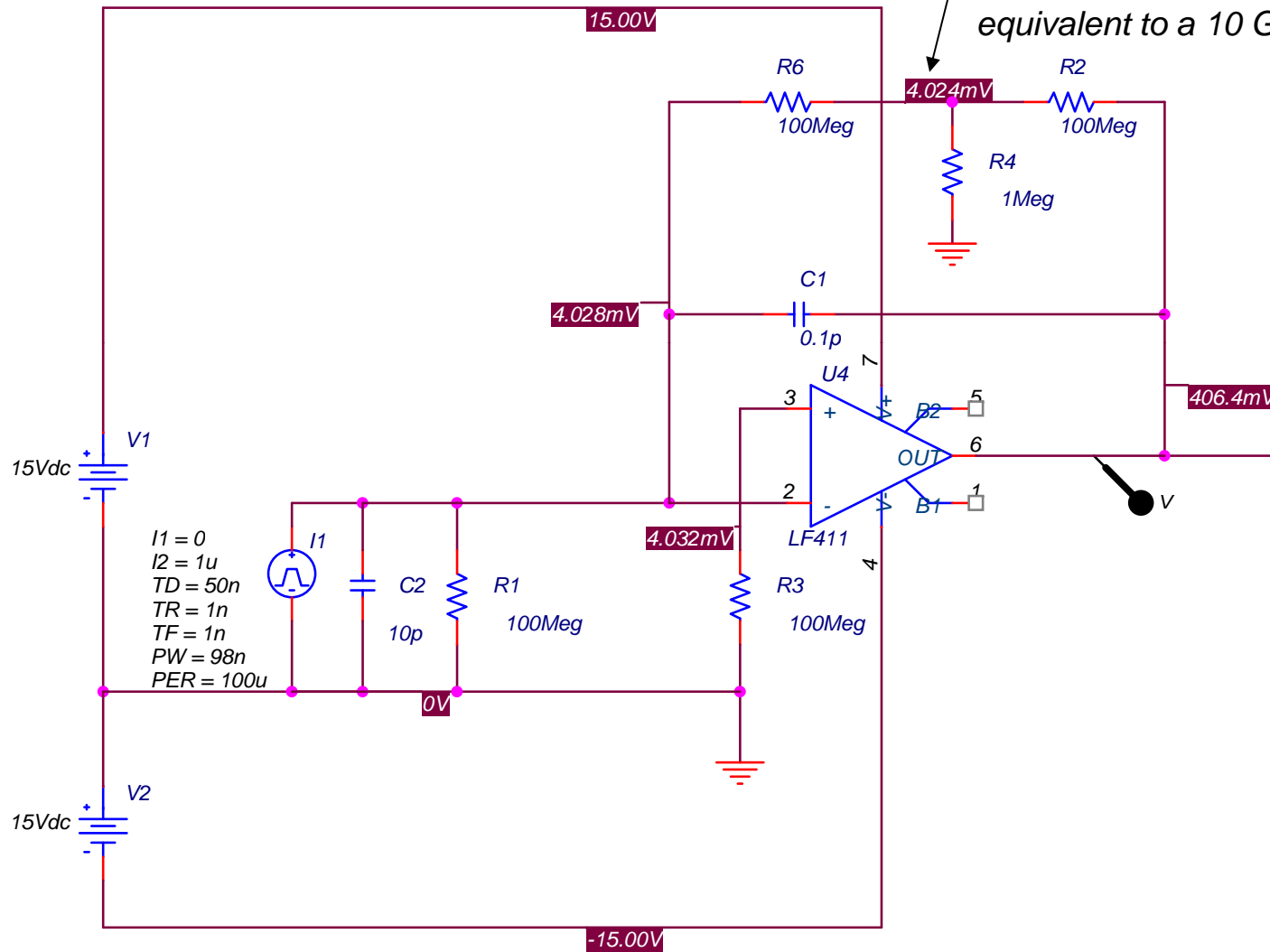Voltage divider divides the output by 100, correspondingly reducing the feedback current. The DC feedback is thus almost equivalent to a 10 Gohm resistor.



Charge Amp with T Network

