

# Physics 160


## Lecture 3

*R. Johnson*

*April 6, 2015*
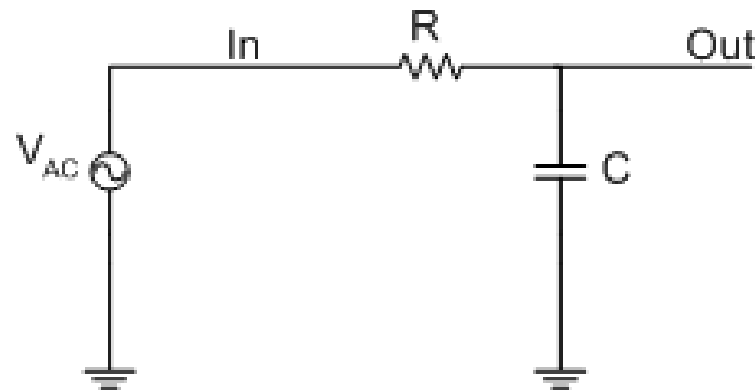
# RC Circuit (Low-Pass Filter)

This is the same RC circuit we looked at earlier in the time domain, but here we are interested in the frequency response. So we input a sine wave instead of a step function.




$$\tau \equiv RC$$

$$I = V_{\text{in}}/Z \quad \text{where} \quad Z = R + \frac{1}{j\omega C} \quad \text{Complex impedance}$$


$$V_{\text{out}} = I \cdot X_C = V_{\text{in}} \cdot \frac{X_C}{Z} = V_{\text{in}} \times \frac{1/j\omega C}{R + 1/j\omega C}$$

$$\text{"gain"} \quad H = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega\tau)^2}} e^{-j\phi} \quad \text{where} \quad \phi = \tan^{-1}(\omega\tau)$$
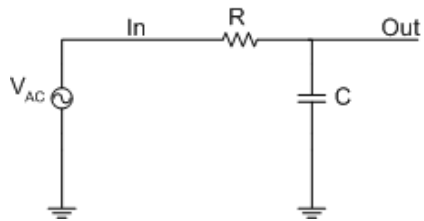
# Low Pass Filter Response ( $V_{out}/V_{in}$ )




$h(\omega)$

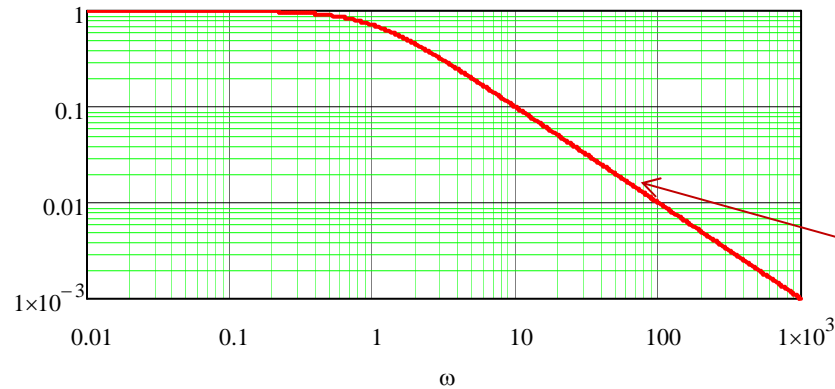

Magnitude

Slope is  $-6$  dB/octave (or  $-20$  dB/decade)

Plotted for  $\tau = 1$

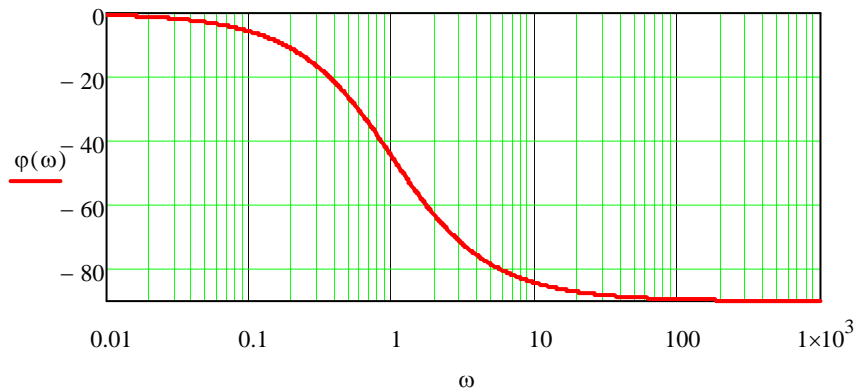


Phase

The “ $-3$ dB point” is where the output falls by  $\frac{1}{\sqrt{2}}$  (power falls by  $1/2$ )

$$20 \log\left(\frac{1}{\sqrt{2}}\right) = -10 \log(2) = -3.01$$

$$\text{-3dB point : } \omega = \frac{1}{\tau} \text{ and } \phi = -45^\circ$$

# Low Pass Filter (single pole) Recap

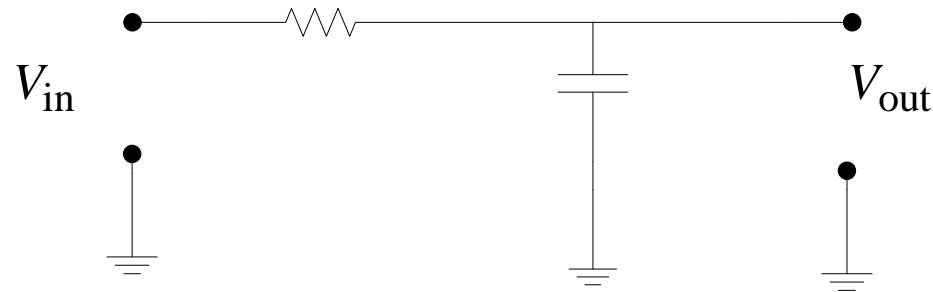

- Also known as an “integrator” (time domain)!
  - Lousy example; we will make nearly perfect integrators from op amps later in the quarter.

- Frequency response:

- 3dB point is at  $f=1/(2\pi RC)$
- $-6\text{dB/octave}$  falloff at high  $f$
- Phase shift ( $V_{out}$  is the voltage across the capacitor):


- $V_{out}$  lags  $V_{in}$
- 0 degrees at low frequency
- 45 degrees at the 3dB point
- 90 degrees at high frequency, far above the 3dB point

$$V_{out} = \frac{1}{C} \int I(t) dt \approx \frac{1}{RC} \int V_{in} dt$$

This is valid for only a short time, while  $V_{out} \sim 0$ .
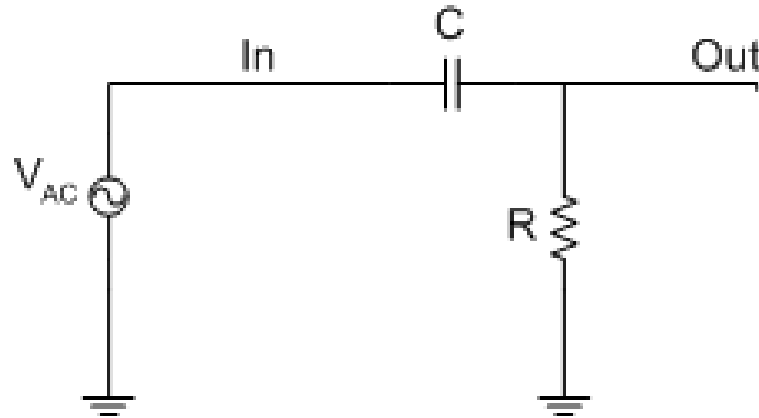
# RC Circuit (High-Pass Filter)

Again just an RC circuit, but we swapped the resistor and capacitor, so that now the output voltage is given by the current through the resistor.





$$\tau \equiv RC$$

$$I = V_{in}/Z \quad \text{where} \quad Z = R + \frac{1}{j\omega C}$$

$$V_{out} = I \cdot R = V_{in} \cdot \frac{R}{Z} = V_{in} \times \frac{R}{R + 1/j\omega C}$$


$$\frac{V_{out}}{V_{in}} = \frac{j\omega\tau}{1 + j\omega\tau} = \frac{1}{1 - j/\omega\tau} = \frac{1}{\sqrt{1 + (1/\omega\tau)^2}} e^{j\phi} \quad \text{where} \quad \phi = \tan^{-1}(1/\omega\tau)$$
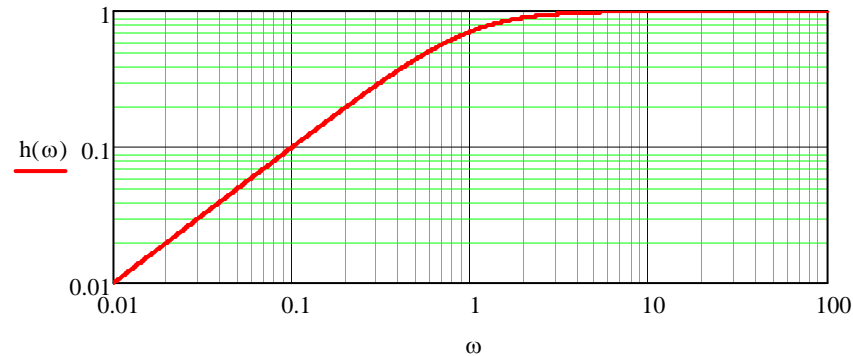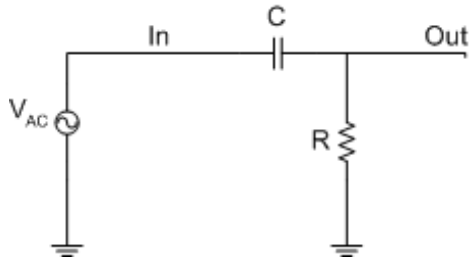
# High Pass Filter Response ( $V_{out}/V_{in}$ )



Magnitude

Plotted for  $\tau = 1$

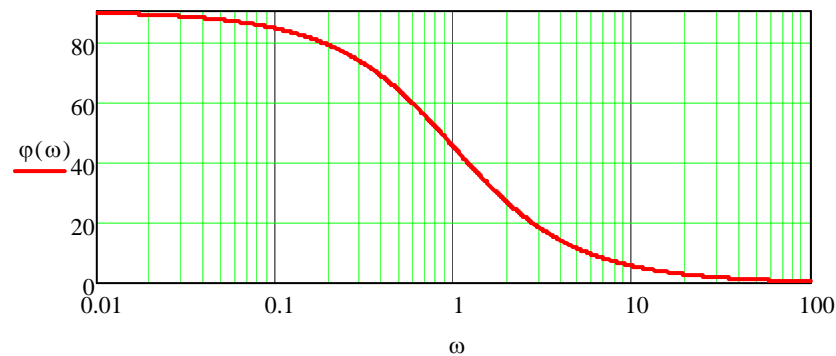


Phase

The “-3dB point” is where the output falls by  $\frac{1}{\sqrt{2}}$  (power falls by  $1/2$ )

$$20 \log\left(\frac{1}{\sqrt{2}}\right) = -10 \log(2) = -3.01$$

$$\text{-3dB point: } \omega = \frac{1}{\tau} \text{ and } \phi = 45^\circ$$


# High Pass Filter (single pole) Recap

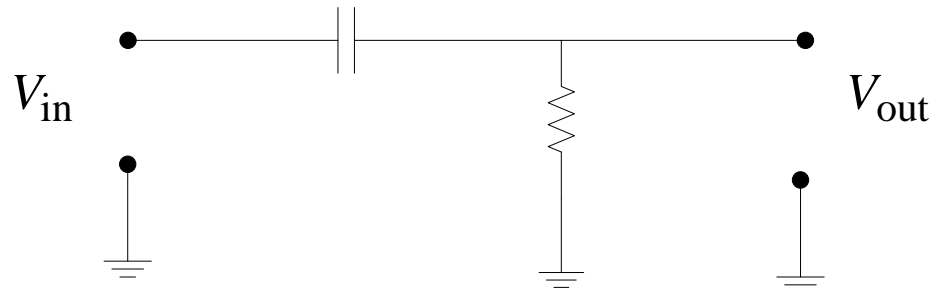

- Also known as a “differentiator” (time domain)!
  - Lousy example; we will make nearly perfect differentiators from op amps later in the quarter.
- Frequency response
$$V_{out} = R \cdot \frac{dQ}{dt} \approx RC \frac{d}{dt} V_{in}$$
  - 3dB point is at  $f=1/(2\pi RC)$
  - 6dB/octave (fancy way of saying unity slope) for low  $f$
  - Phase shift ( $V_{out}$  is proportional to the current in  $R$ )
    - $V_{out}$  leads  $V_{in}$
    - 0 degrees at high frequency
    - 45 degrees at the 3dB point
    - 90 degrees far below the 3dB point

This is valid for only a short time, while  $V_{out} \sim 0$ .

## Inductor (AC Steady State)

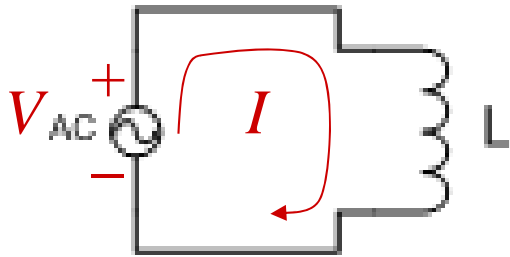



$$I = I_0 \sin \omega t = I_0 \cos(\omega t - \frac{\pi}{2})$$

$$V + \left( -L \frac{dI}{dt} \right) = 0 \quad \text{Kirchhoff loop rule}$$

$$V = L \frac{dI}{dt} = \omega L \cdot I_0 \cos \omega t$$

$$V = \omega L \cdot I_0 \cos \omega t$$

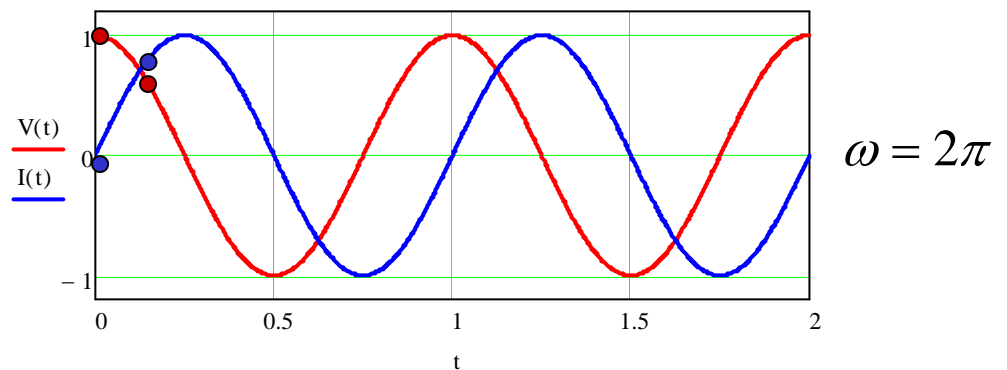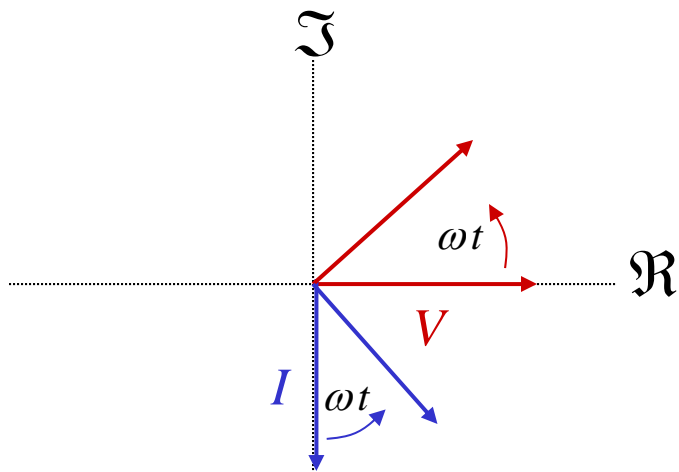Current *lags* voltage by  $\frac{1}{4}$  period ( $90^\circ$ )



“Phasors”: The real part traces out the cosine curves as the vector rotates.



## Phasors are Complex Numbers


Physical voltage and current are understood to be the real part of the complex quantity.

The real and imaginary parts don't get mixed up by the circuit equations *as long as the circuit is linear*.

$$I = I_0 \cos(\omega t - \frac{\pi}{2}) = \Re \left\{ -j \cdot I_0 e^{j\omega t} \right\} \quad \left( -j = -\sqrt{-1} = e^{-j\frac{\pi}{2}} \right)$$

$$V = \omega L \cdot I_0 \cos \omega t = \Re \left\{ j\omega L \cdot (-j I_0 e^{j\omega t}) \right\}$$

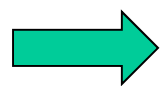Considering  $I$  and  $V$  to be complex numbers:



$$V = I \cdot Z$$

$$Z = j\omega L$$

“Impedance”

# Summary

All 3 linear circuit elements provide an “impedance” ( $Z$ ) to the flow of current, but one has to specify a phase difference between current and voltage as well as a change in amplitude.

Assume that the voltage is given by  $V(t) = V_0 e^{j\omega t}$

$$I(t) = I_{\max} e^{j\phi} e^{j\omega t}$$


*I and V in phase*



$$I(t) = \frac{V_0}{R} e^{j\omega t}$$

$$Z = R \text{ and } \phi = 0$$

*I leads V by 90°*

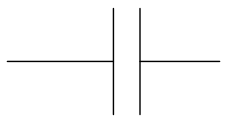

$$I(t) = \frac{V_0}{1/j\omega C} e^{j\omega t}$$

“Reactance:”

$$Z = X_C = \frac{1}{j\omega C} \text{ and } \phi = +\frac{\pi}{2}$$

*I lags V by 90°*




$$I(t) = \frac{V_0}{j\omega L} e^{j\omega t}$$

$$Z = X_L = j\omega L \text{ and } \phi = -\frac{\pi}{2}$$
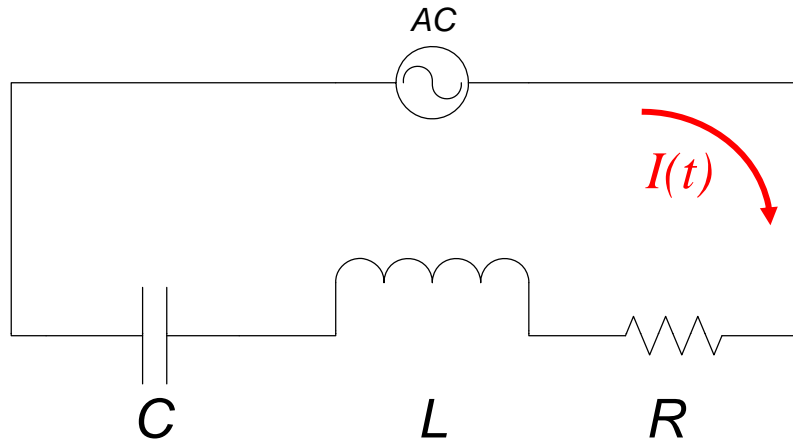
## Series LCR Circuit (Physics 5C)

$$V_s(t) = V_0 \cos \omega t = \Re(V_0 e^{j\omega t})$$



$$I(t) = \Re\left(I_{\max} e^{j(\omega t + \phi)}\right)$$

$$I_{\max} = \frac{V_0}{|Z|}$$


$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad \text{is minimum when } \omega L = \frac{1}{\omega C} \quad \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\phi = -\tan^{-1}\left(\frac{\omega L - 1/\omega C}{R}\right) = 0 \quad \text{when } \omega = \frac{1}{\sqrt{LC}} \quad \longrightarrow \quad I(t) = \frac{V_0}{R} \cos \omega t$$

*Maximum current*

[http://vnatsci.ltu.edu/s\\_schneider/physlets/main/rlc.shtml](http://vnatsci.ltu.edu/s_schneider/physlets/main/rlc.shtml)

# Resonance in a Series LCR Circuit

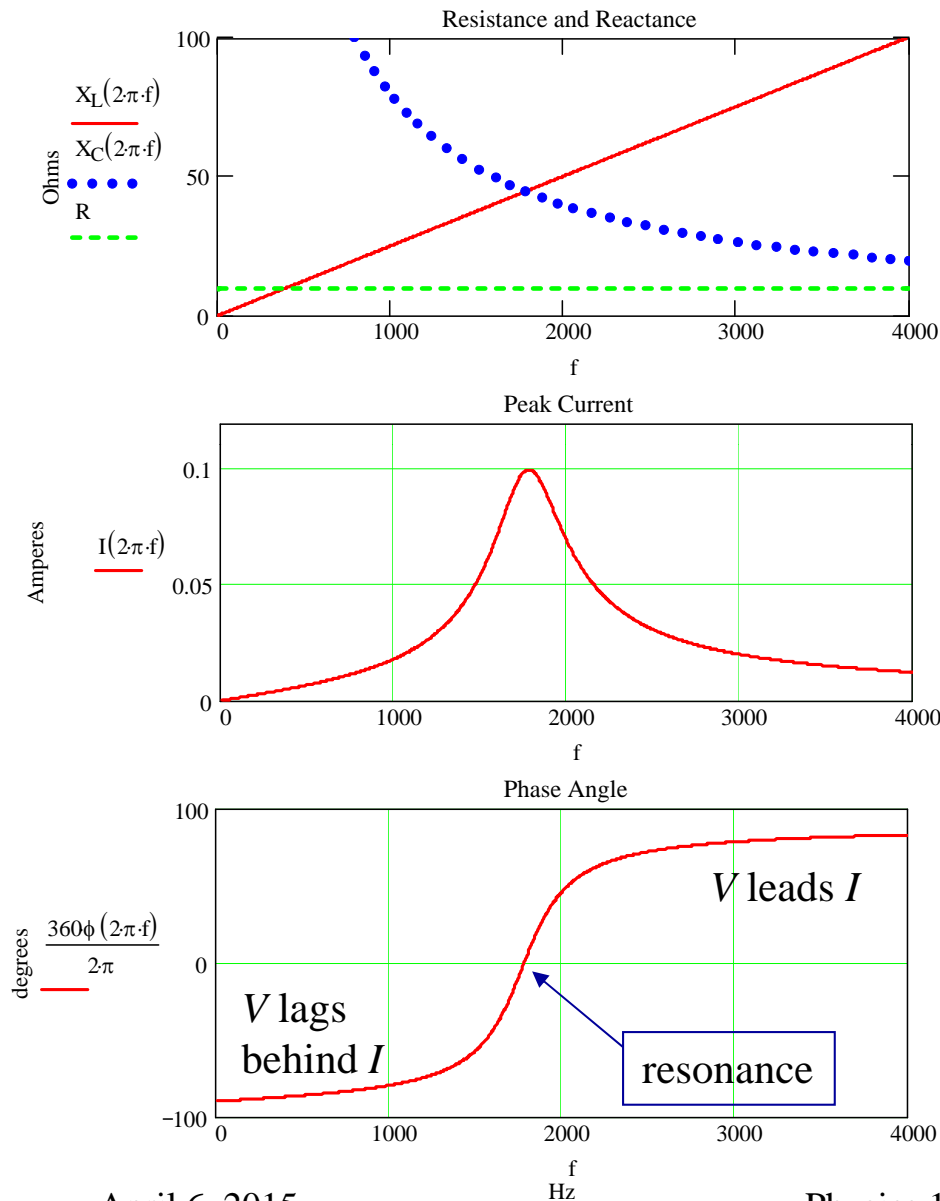

At resonance:

1. The inductive and capacitive reactances are equal in magnitude.
2. The current is maximum.
3. The phase angle between voltage and current is zero.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

At low  $f$ , the circuit looks  $RC$ .  
At high  $f$ , the circuit looks  $RL$ .

# Power

$$P(t) = I(t) \cdot V(t)$$

But usually we measure the *average* power.




$$\bar{P} = \frac{1}{T} \int_0^T I(t) \cdot V(t) dt = \frac{1}{2} \Re\left(IV^*\right) = I_{\text{rms}} V_{\text{rms}} \cos \phi$$

Complex amplitudes                      “Power factor”

Where phi is the phase difference between the voltage and current.

- $\phi=0$  for resistor (max. power)
- $\phi=\pi/2$  for capacitor (zero power)
- $\phi=-\pi/2$  for inductor (zero power)

# Resonance in a Series LCR Circuit

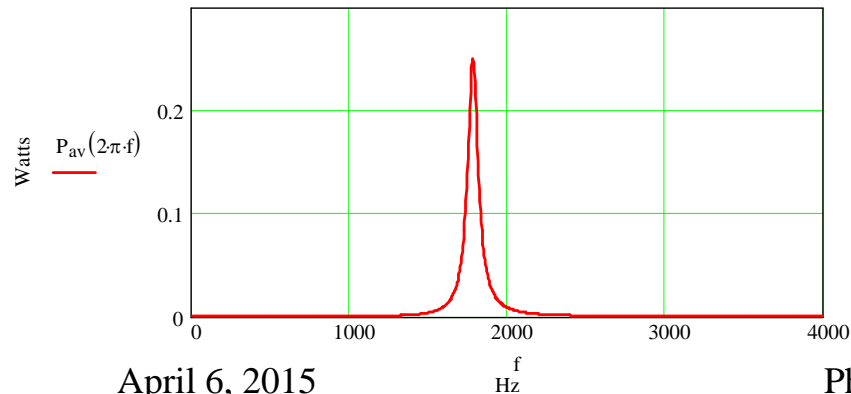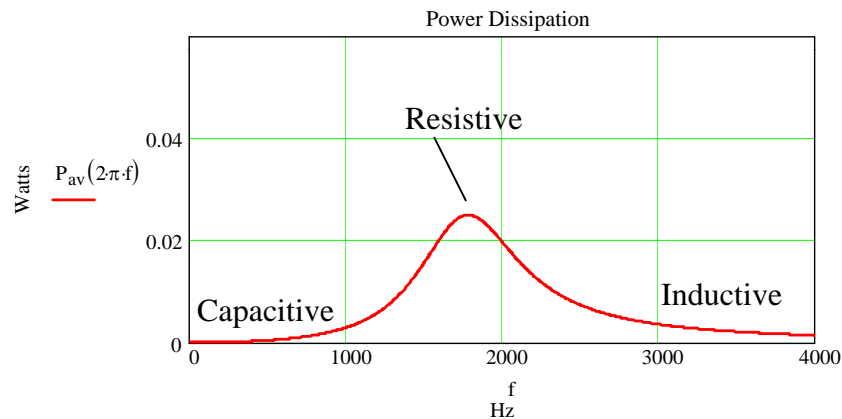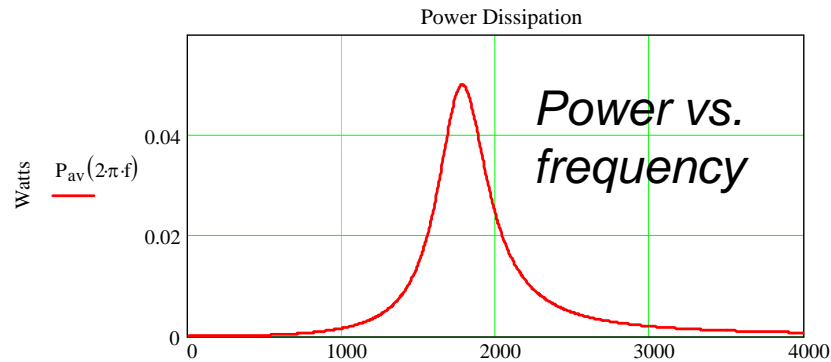


*Large damping gives a broad low resonance.*

*Small damping gives a sharp, high resonance (good for a radio receiver).*
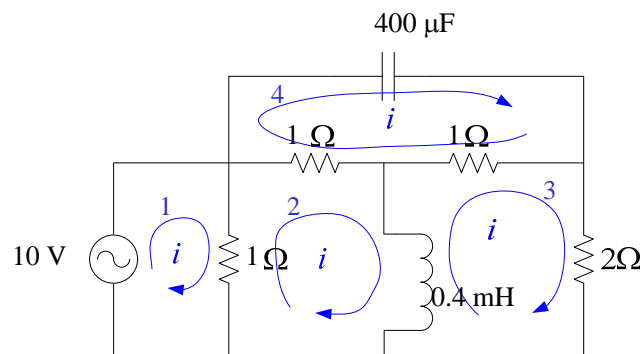
# More Elaborate LRC Networks

- *Straight-forward application of complex impedance, resulting in simultaneous complex equations.*
  - *Easy to solve with a computer (but messy by hand).*
  - *See example in handout.*
- *But for most of this course we really only need the two simple RC filters!*



$$V=10 \text{ V}$$


$$\omega=10^4 \text{ rad/s}$$

$$\begin{pmatrix} 1 & -1 & 0 & 0 \\ 1 & -2-4j & 4j & 1 \\ 0 & 4j & -3-4j & 1 \\ 0 & 1 & 1 & -2+0.25j \end{pmatrix} \times \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \\ 0 \\ 0 \end{pmatrix} \quad \longrightarrow \quad I = \begin{pmatrix} 15.457 - 1.787j \\ 5.457 - 1.787j \\ 4.990 + 0.652j \\ 5.213 + 0.084j \end{pmatrix}$$

Impedance seen by the source:  $Z_{\text{eq}} = \frac{V}{i_1} = \frac{10}{15.56} \cdot e^{+j0.037\pi}$

# AC (linear) Analysis with PSpice

- See the PSpice tutorial and HW #1.

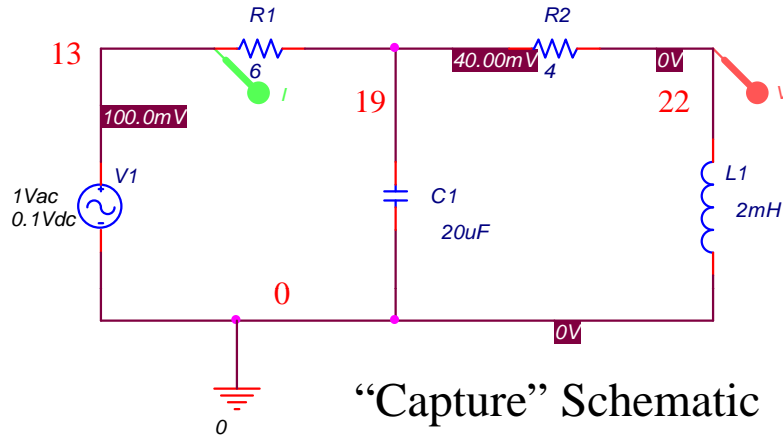

“Capture” Schematic

$$\frac{1}{2\pi\sqrt{LC}} = 796 \text{ Hz}$$

PSpice Output  
(AC Analysis)

## PSpice Netlist

V_V1	N00013	0	DC 0.1Vdc	AC 1Vac
R_R1	N00013	N00019	6	
R_R2	N00019	N00022	4	
L_L1	0	N00022	2mH	
C_C1	0	N00019	20uF	

