

PHYSICS 110B SPRING 2003

MIDTERM I

PUT YOUR NAME ON THE EXAM RIGHT AWAY!

PROBLEM 1 [25 POINTS]

A long straight wire contains a net electrical charge of λ C/m. This wire runs down the axis of an infinite solenoid of radius s_0 , which is wound with n turns per meter. Calculate the total momentum and angular momentum (magnitude and direction, in both cases) carried in the fields in a length z_0 of this configuration, assuming that a current I courses through the turns of the solenoid. Angular momentum is only defined up to a chosen axis; let the axis of choice be the obvious one; i.e., the axis of the solenoid along which the wire lies.

PROBLEM 2 [25 POINTS]

An infinite straight wire carries a current I_0 . A square loop of wire of side a rests with its near edge a distance a from the wire (see diagram). At $t = 0$ the current in the straight wire is switched off, and it dies away with a time-dependence of

$$I(t) = I_0 e^{-t/\alpha}.$$

If the total resistance in the square loop is R , what is the total energy dissipated by the loop as the current in the wire dies away? You may ignore the self-inductance of the loop. (Remember, of course, that the rate of energy dissipated by a resistor is $P = \varepsilon^2/R$, where ε is the emf across the resistor).

PROBLEM 3 [25 POINTS]

A voltage source $V_s(t) = V_0 \cos(\omega t)$ drives a series L – R circuit (no capacitance in the circuit). The values of the resistance and inductance are 6Ω and 10 mH (10^{-2} Henry), respectively.

- a) Assuming $V_0 = 10$ Volts, at what angular frequency ω is the amplitude of the current oscillation through the circuit exactly 1 Amp?
- b) What is the average power delivered by the voltage source into the circuit?

PROBLEM 4 [25 POINTS]

A perfectly-coupled unit-gain transformer (i.e., a transformer with $L_1 = L_2 = L$ and $M = L$) is driven by a source voltage

$$V_s = V_0 \cos(\omega t).$$

Both the primary and secondary coil are encumbered by equal purely resistive loads of magnitude R . In addition, the secondary inductor is leaky, meaning it is effectively connected in parallel with a parasitic resistance R_p (see diagram).

To make the following calculation more tractable, please assume that $R_p = R$, and that the oscillation frequency is set so that $\omega L = R$.

Your task: solve for the amplitude I_L of the current oscillation through the load of the secondary coil, as a function of V_0 and R .